

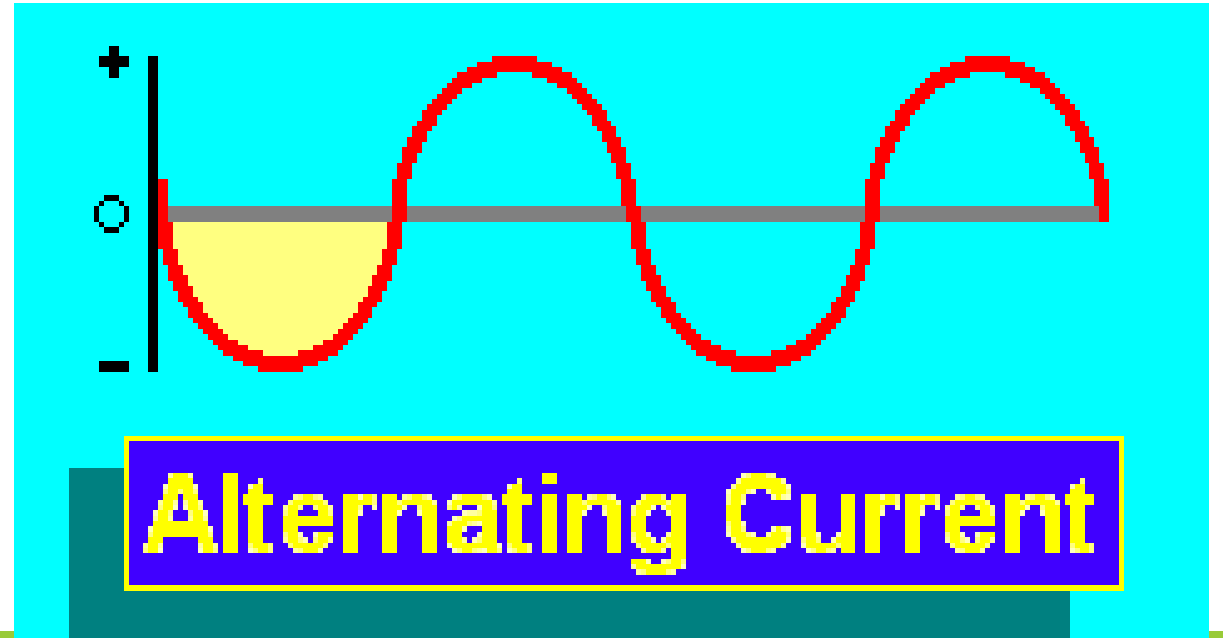
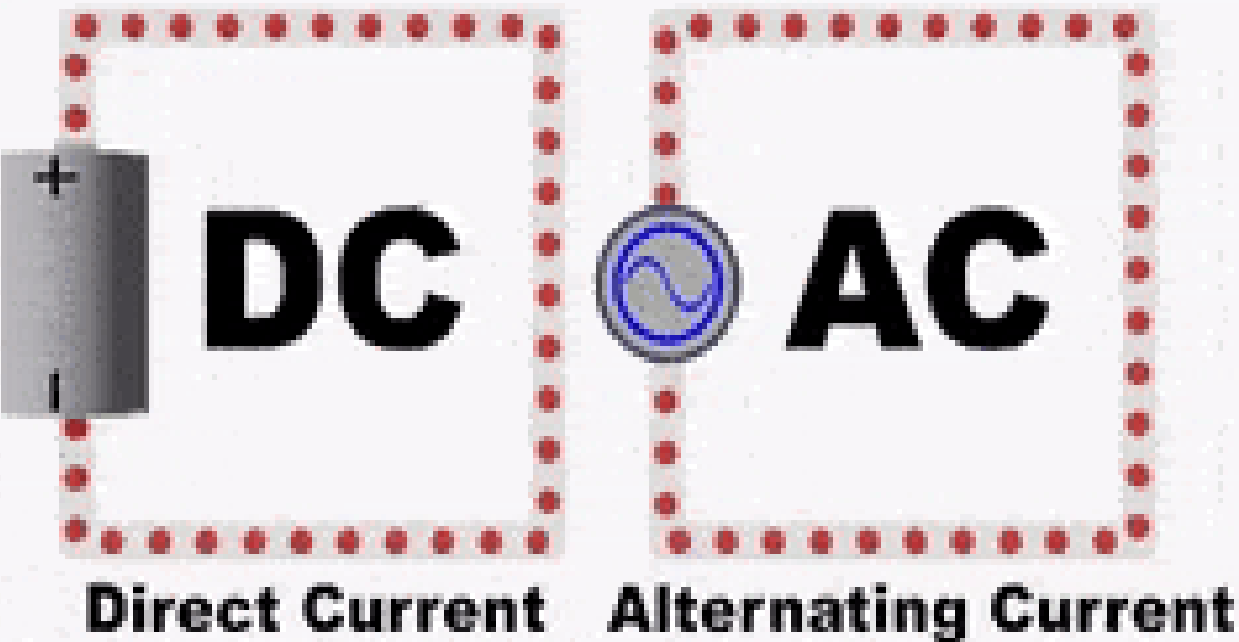

 
# Module 2. A.C.Fundamentals

- Alternating quantity
- Instantaneous signal
- Sinusoidal signal



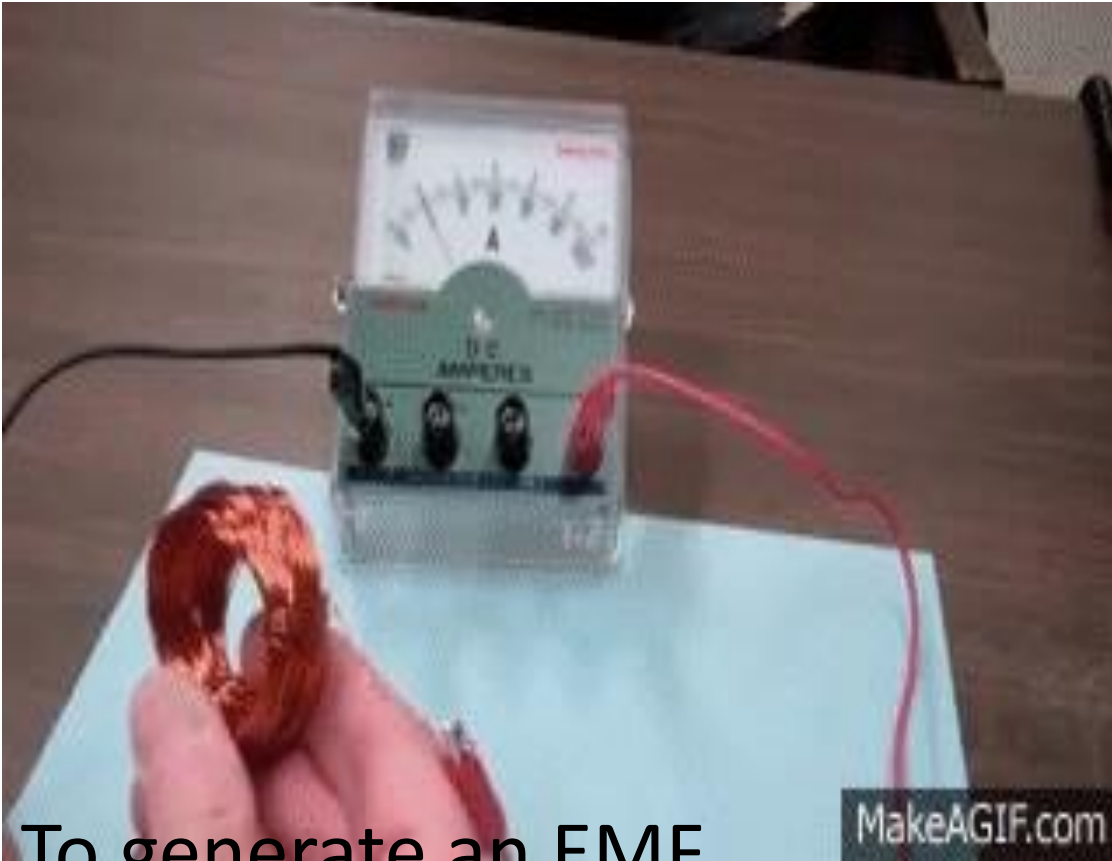
# Faradays laws of Electromagnetic Induction



To generate an EMF

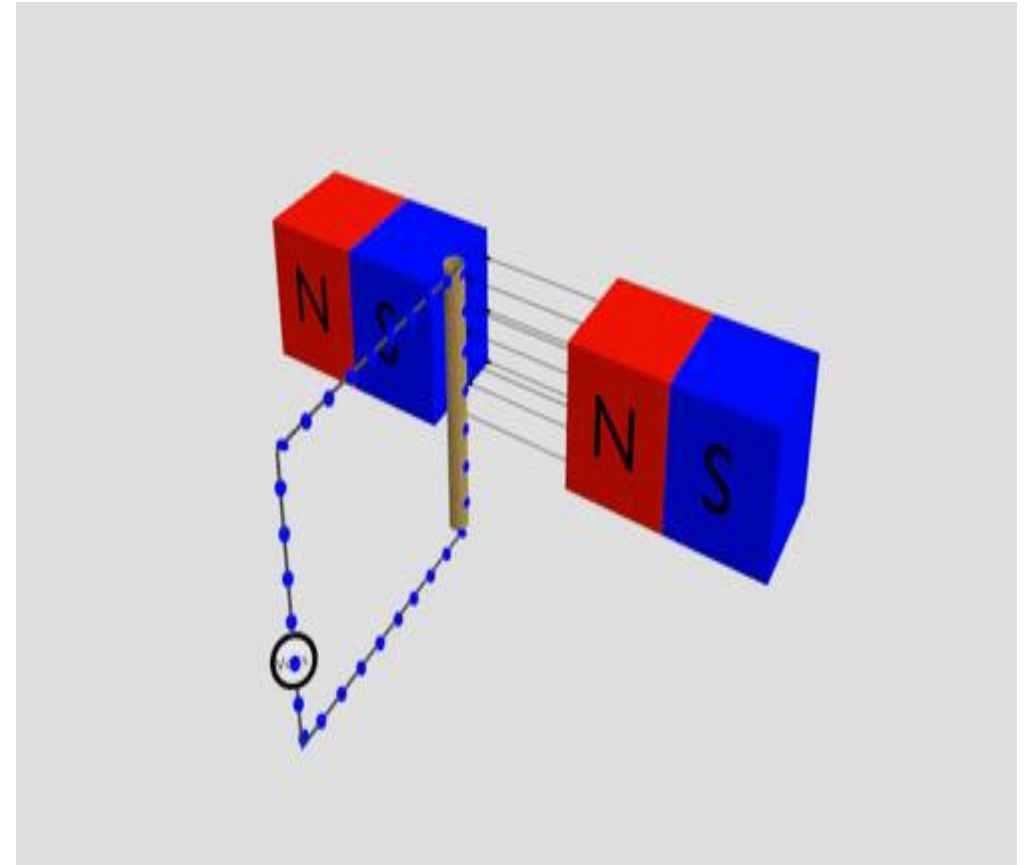1. Magnetic Field
2. Conductor
3. Relative motion between the conductor.



**Whenever a conductor is placed in a varying magnetic field, an EMF is induced in a conductor.**


**Dynamically Induced Emf**

$$e = B l v \sin\theta \quad \text{volts}$$

- where  $B$  - Flux density of the magnetic field in  $\text{wb/m}^2$
- $l$  - Length of the conductor in m
- $v$  - velocity of the conductor in m/s
- $\theta$  - angle between the relative velocity of the conductor and the plane of the flux.
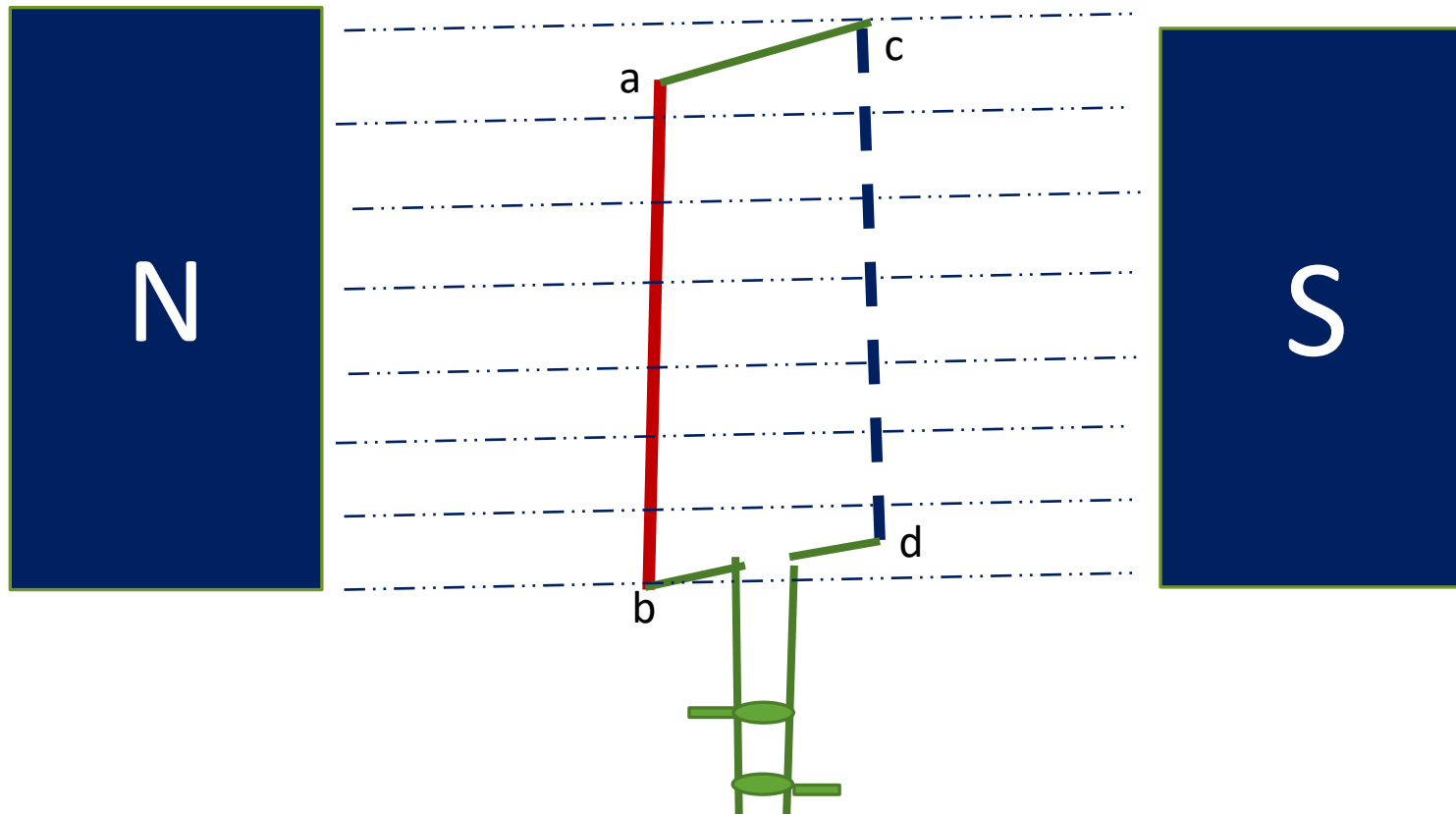
# Generation of AC voltage

- Consider a rectangular coil placed in a uniform magnetic field produced by two poles as shown in the figure.




- Rotate the coil in the anticlockwise direction ,while rotating the conductors will cut the magnetic flux due to which an emf is Induced in the conductor . The magnitude of the Induced Emf is depends upon the position of the conductor in an magnetic Field.
- We know the from the faraday's laws of electromagnetic Induction
- The dynamically Induced Emf is given by

$$e = B l v \sin\theta \quad \text{volts}$$

- where  $B$  - Flux density of the magnetic field in  $\text{wb/m}^2$
- $l$  - Length of the conductor in m
- $v$  - velocity of the conductor in  $\text{m/s}$
- $\theta$  - angle between the relative velocity of the conductor and the plane of the flux.

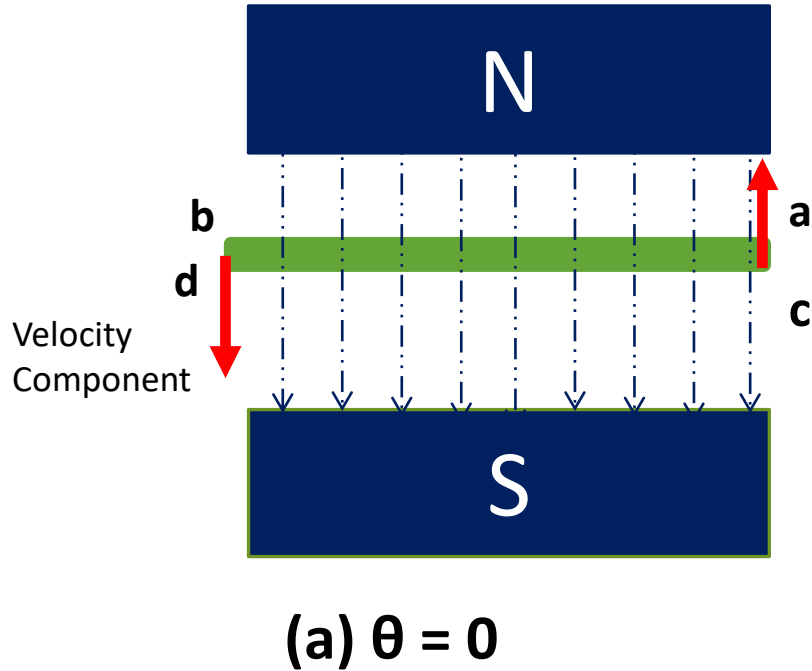
- Let the Initial position of the coil be as shown in fig a.



- The angle between the magnetic flux and velocity component is zero i.e.  $\theta = 0$ .
- Hence the Emf Induced

$$e = B l v \sin 0 = 0 \quad \text{--- zero Emf}$$

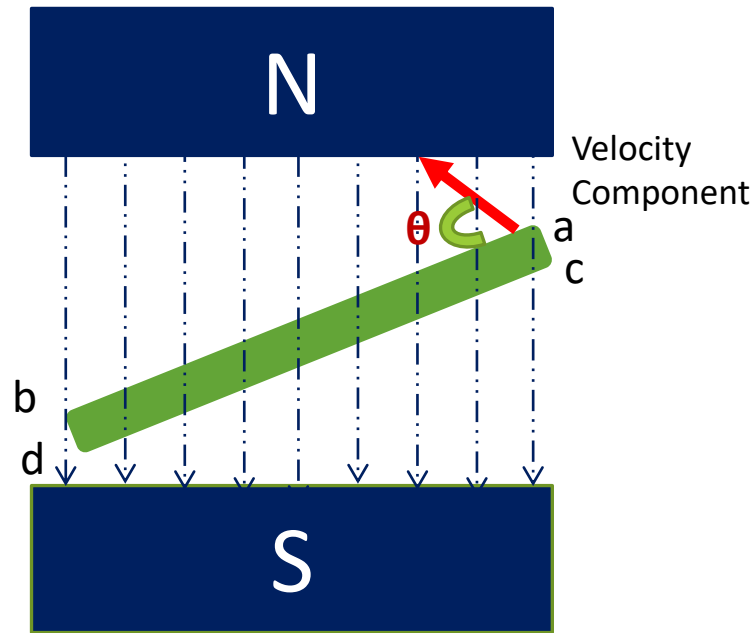- When the coil is rotated in anticlockwise direction through some angle  $\theta$  as shown in fig b.



(b)  $(0 < \theta < 90)$


- The instantaneous component of velocity of conductors is cutting the flux with an angle  $\theta$ .

- Hence the Emf Induced

$$e = B l v \sin \theta \quad \text{-----} (0 < \theta < 90)$$

ex:  $\theta$  is 30 then  $e = 0.5 Blv$

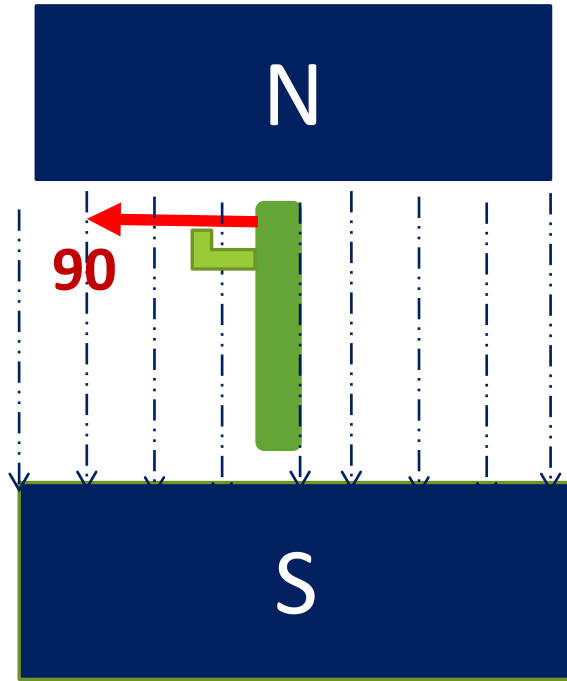When the coil is further rotate in an anticlockwise direction ,the instantaneous component of velocity acting perpendicular to the line of the flux as shown in fig c.




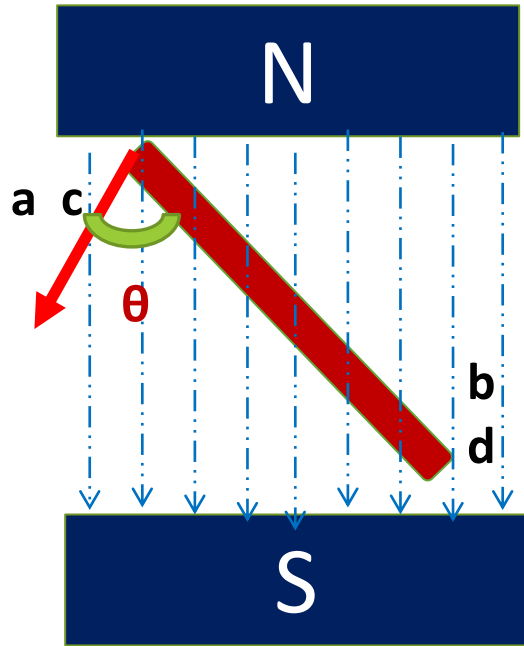(c)  $\theta = 90$

- Therefore the angle between the magnetic flux and velocity component is  $90^\circ$ , i.e.  $\theta = 90^\circ$ .
- Hence the Emf Induced
$$e = B l v \sin 90^\circ = Blv$$
- So the Induced emf in this position is at its maximum Value.



Lets consider other Instants of coil as shown in Fig d,e and f .




**(d)  $(90 < \theta < 180)$**

$$e = B l v \sin \theta$$


**Ex : if  $\theta = 150$**

$$e = 0.5 B l v$$

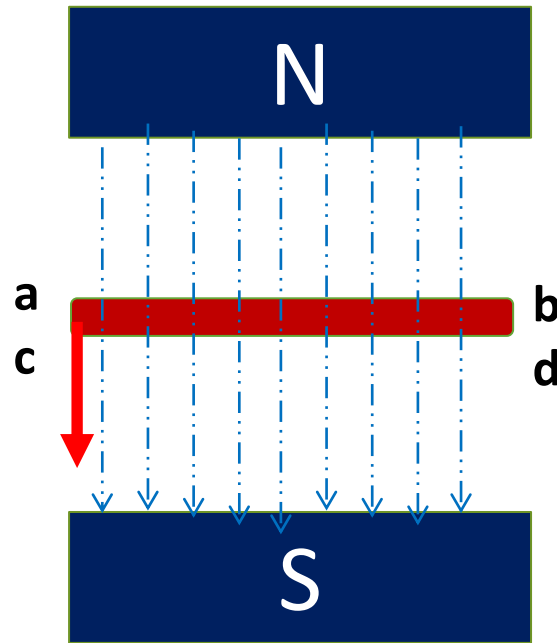

**(e)  $\theta = 180$**

$$e = 0$$

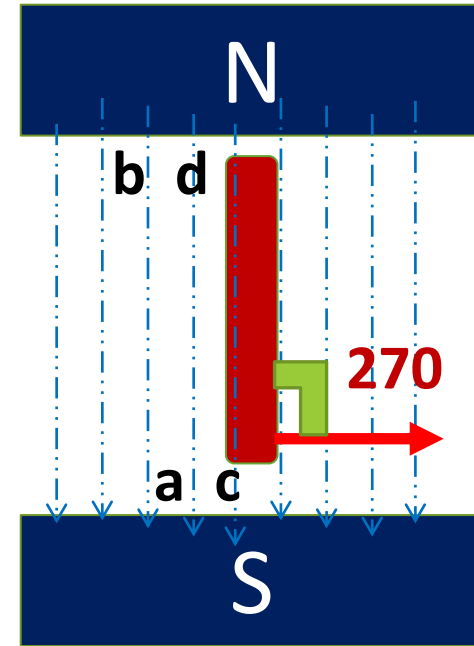


**(f)  $\theta = 270$**



$$e = -B l v$$

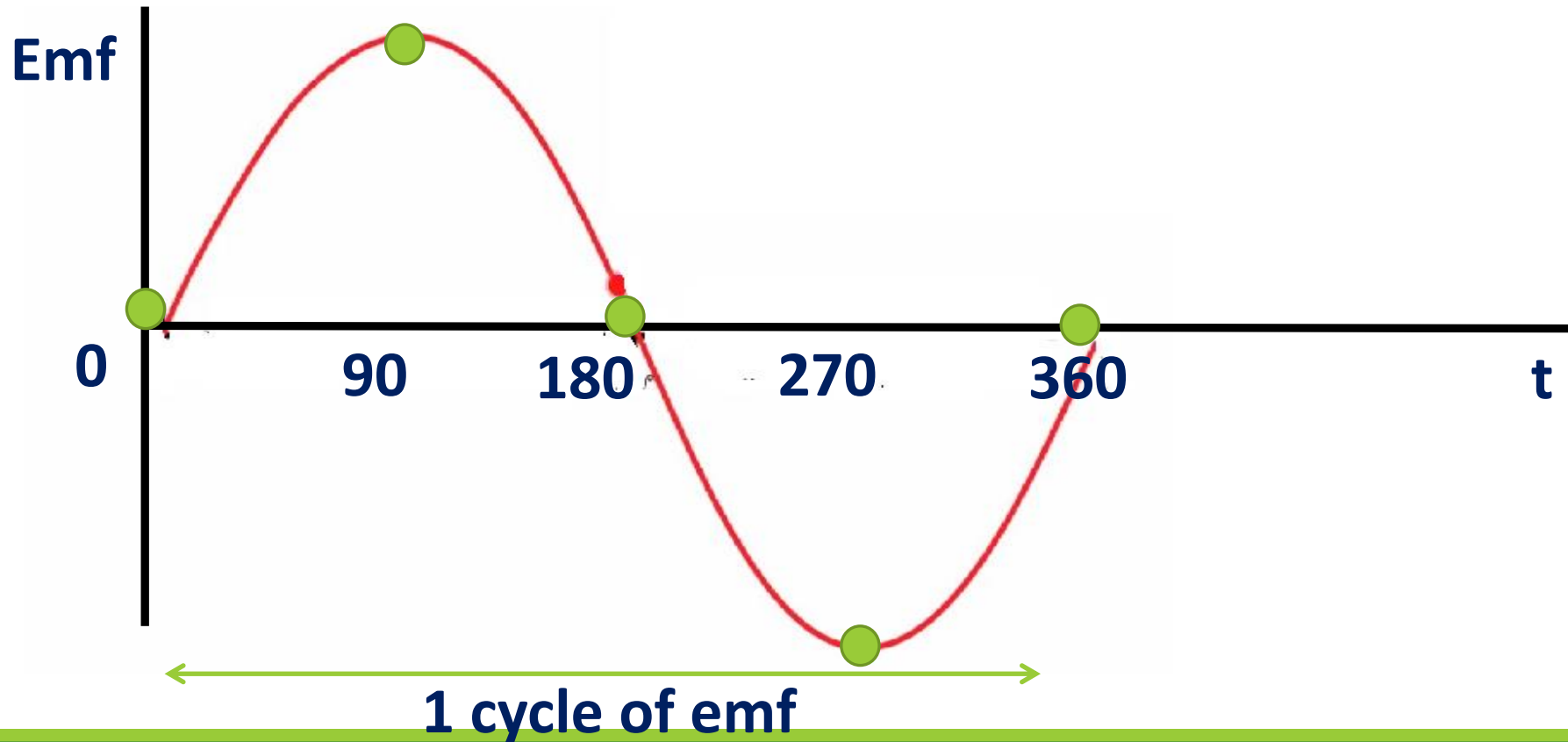**Similarly when  $\theta = 360$  then  $e = 0$**

So, when  $\theta$  varies from 0 to 360 the emf in an conductor varies in an alternating manner I,e from zero to maximum in one direction ,decreasing to zero, then achieving maximum in another direction and again decreasing to zero.

Therefore by rotating conductor from 0 to 360 we get one cycle of emf




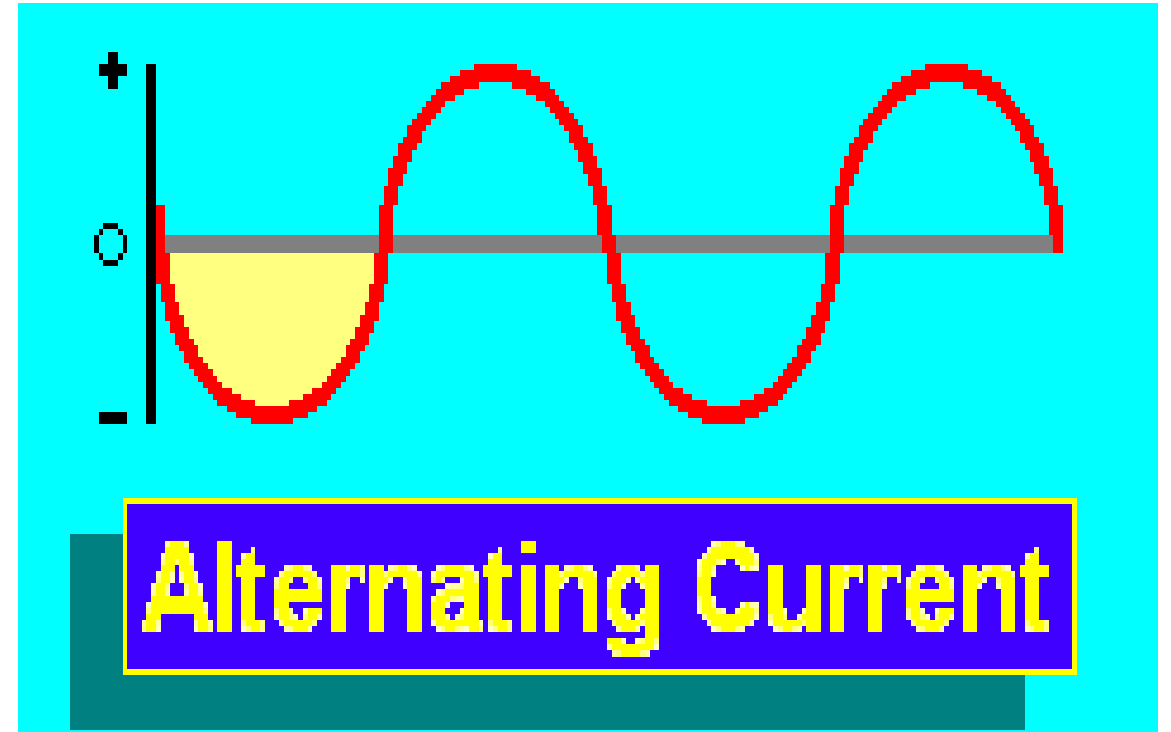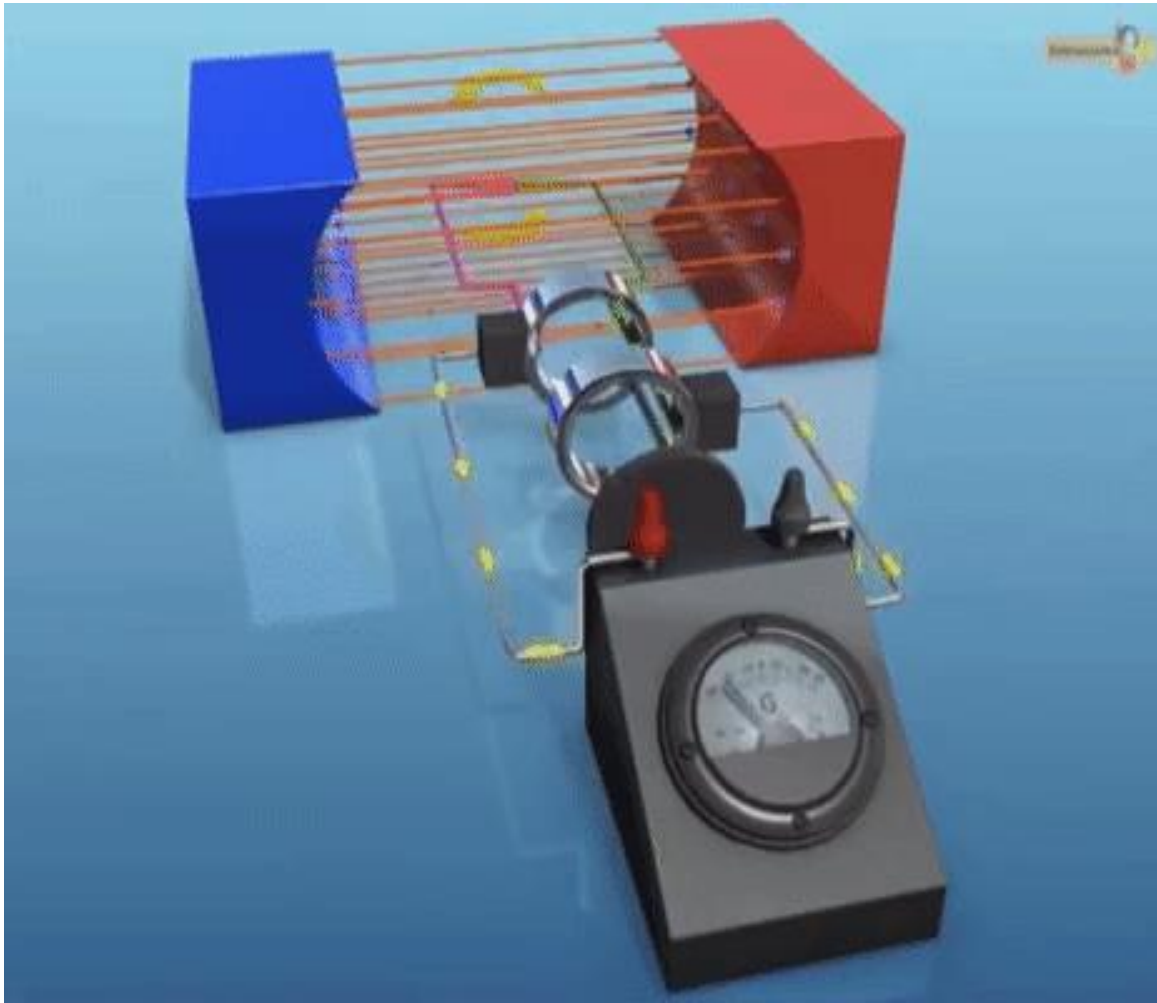

# Advantages of AC system over DC system

1. AC voltages can be efficiently stepped up/down using a device transformer.
2. By increasing the transmission voltage the losses can be reduced.
3. AC machines are simpler in construction than DC machines.
4. The cost and maintenance of AC machines are less compared to DC machines.
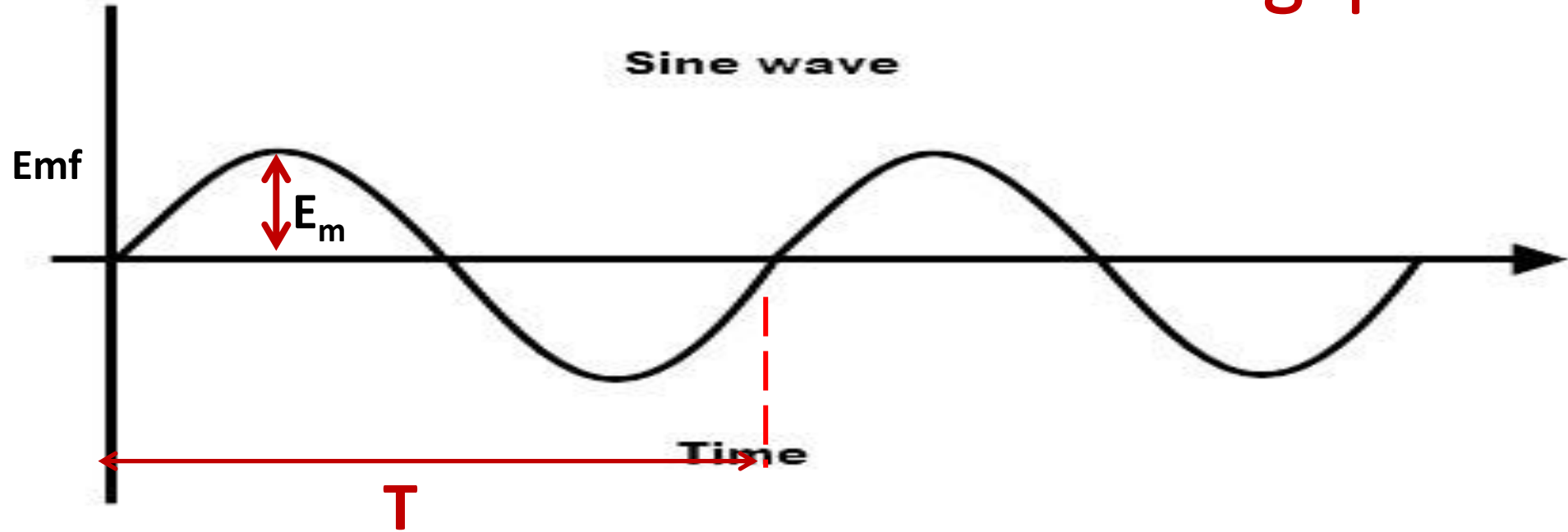
# Important terms associated with an alternating quantity



**Amplitude ( $E_m$  or  $I_m$ ):** It is the maximum value attained by an alternating quantity. Also called as maximum or peak value.

**Time Period ( $T$ ):** It is the Time Taken to complete one cycle of an alternating quantity.

**Instantaneous Value ( $e$  or  $i$ ):** It is the value of the quantity at any instant.

$$e = Blv \sin \theta \quad \text{wkt } E_m = Blv$$

$$e = E_m \sin \theta \text{ or } E_m \sin \omega t \quad \text{and} \quad i = I_m \sin \theta \text{ or } I_m \sin \omega t$$

**4. Frequency (f):** It is the number of cycles completed by alternating quantity in one second.

The unit for frequency is **Hz or cycles/sec.**

$$T = 1/f \text{ ----sec}$$

**5. Angular Frequency ( $\omega$ ):** Angular frequency is defined as the number of radians covered in one second.

The unit of angular frequency is rad/sec.

$$\omega = 2\pi f \text{ -----r/s}$$

**6. Average Value( $E_{av}$  or  $I_{av}$ ):** The arithmetic average of all the values of an alternating quantity over one cycle is called its average value.


$$\text{Average value} = \frac{\text{Area under curve half cycle}}{\text{length of base over half cycle}}$$

$$I_{av} = \frac{2I_m}{\pi} = 0.637I_m$$

$$E_{av} = \frac{2E_m}{\pi} = 0.637E_m$$
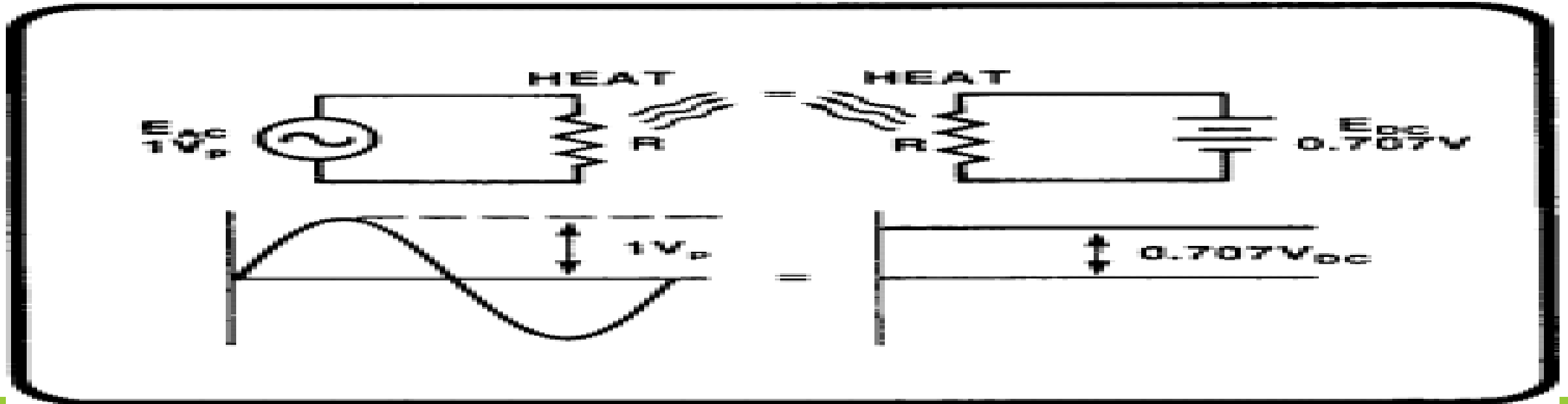
# RMS(Root mean square) or Effective Value( $E_{rms}$ or $I_{rms}$ )

**Definition:** The effective or RMS value of an alternating quantity is that steady current (dc) which when flowing through a given resistance for a given time produces the same amount of heat produced by the alternating current flowing through the same resistance for the same time.





$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}} = 0.707I_m$$

$$E_{\text{rms}} = \frac{E_m}{\sqrt{2}} = 0.707E_m$$

**Form Factor ( $K_f$ ):** The Form factor of an alternating quantity is defined as the ratio of Rms value to the average value.

$$K_f = \frac{\text{RMS value}}{\text{Average value}}$$

The form factor of alternating current can be obtained as

$$K_f = \frac{0.707I_m}{0.637I_m} = 1.11$$

**Crest or Peak Factor ( $K_p$ ):** The peak factor of an alternating quantity is defined as the ratio of maximum value to the RMS value.

$$K_p = \frac{\text{Maximum value}}{\text{RMS value}}$$

The peak factor of alternating current can be obtained as

$$K_p = \frac{I_m}{0.707I_m} = 1.414$$

# Formulas

## 1. Instantaneous Value

$$\begin{aligned} e &= E_m \sin\theta & \text{and} & \quad i = I_m \sin\theta \\ e &= E_m \sin\omega t & \text{and} & \quad i = I_m \sin\omega t \end{aligned}$$

## 2. Time period $T=1/f$ sec

## 3. Angular Frequency $\omega = 2\pi f$ rad/sec

## 4. Average Value

$$I_{av} = \frac{2I_m}{\pi} = 0.637I_m$$

## 5. Rms value

$$I_{rms} = \frac{I_m}{\sqrt{2}} = 0.707I_m$$

## 6. Form factor $K_f = \frac{RMS \text{ value}}{Average \text{ value}}$

## 7. crest or peak factor $K_p = \frac{Maximum \text{ value}}{RMS \text{ value}}$

## Problems

1. The equation of an alternating current is given by  $i = 42.42 \sin 568 t$ . Calculate its i) Maximum Value ii) Frequency iii) Rms value iv) Average value v) form factor vi) peak factor.

Solution:

Given -

$$i = 42.42 \sin 568 t$$

Compare the equation with

$$i = I_m \sin \omega t$$

We get Maximum value

$$I_m = 42.42 \text{ A}$$

and  $\omega = 568$

Wkt  $\omega = 2\pi f$

$$\text{ii) } f = \frac{\omega}{2\pi} = \frac{568}{2 \times 3.14} = 90.42 \text{ Hz}$$

$$\text{Frequency } f = 90.42 \text{ Hz}$$

iii) Rms value  $I_{rms} = 0.707 I_m = 0.707 \times 42.42$

$$I_{rms} = 30A$$

iv) Average value  $I_{av} = 0.637 I_m = 0.637 \times 42.42 = 27.02 A$

$$I_{av} = 27.02A$$

v) Form factor  $K_f = \frac{RMS\ value}{Average\ value} = \frac{30}{27.02} = 1.11$

vi) peak factor  $K_p = \frac{Maximum\ value}{RMS\ value} = \frac{42.42}{30} = 1.414$

The equation of an alternating current is given by  $i = 414 \sin 628 t$   
find i) Max value ii) frequency iii) RMS value  
iv) Average value V) Instantaneous value of current at  $t = 5 \text{ ms}$

The equation for an AC voltage is given as  $V = 0.04 \sin(2000t + 60^\circ) \text{V}$ . Determine the frequency, the angular frequency, instantaneous voltage when  $t = 160 \mu\text{s}$ . What is the time represented by a  $60^\circ$  phase angle. (06 Marks)

**Solution:  $v = 0.04 \sin(2000t + 60) = V_m \sin(\omega t + \phi)$**

**$\omega = 2000 \text{ r/s}$        $V_m = 0.04 \text{ v}$**

**$f = \omega / 2\pi = 2000 / 2 * 3.142 = 318.47 = 319 \text{ Hz}$**

Instantaneous value  $v = ?$  At  $t = 160 \times 10^{-6}$

**$v = 0.04 \sin(2000t + 60)$**

**$v = 0.04 \sin(2000 \times 160 \times 10^{-6} + 1.047) = 0.00095 \text{ V}$**

**$t = ?$        $\phi = \omega t$        $60 = 2000 t$        $t = 0.03 \text{ s}$**



3. For the current wave shown in the fig

Find its i) Peak Value ii) Periodic time iii) Frequency iii) Rms value iv) Average value v) form factor v) peak factor vi) instantaneous value at  $t=3\text{ms}$

Solution: From the fig

i) Peak Value


$$I_m = 20\text{A}$$

ii) Periodic Time

$$T = 1/100 = 0.01 \text{ sec}$$

iii) Frequency  $f = 1/T = 1/0.01 = 100\text{Hz}$

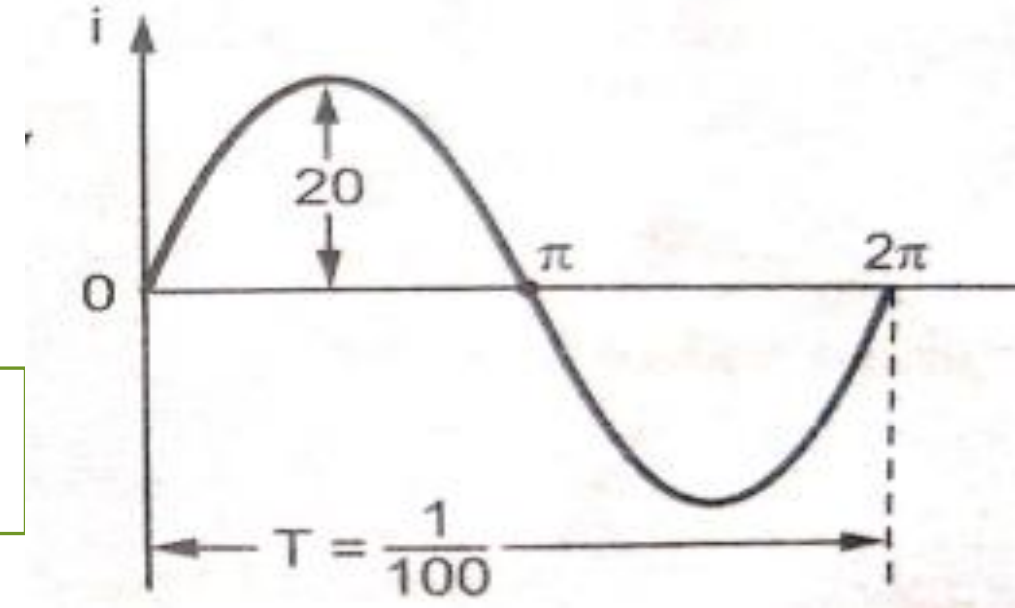iv) Rms value  $I_{rms} = 0.707 I_m = 0.707 \times 20 = 14.14 \text{ A}$



iv) Average value  $I_{av} = 0.637 I_m = 0.637 \times 20 = 12.74 A$

$$I_{av} = 12.74A$$

v) Form factor  $K_f = \frac{RMS\ value}{Average\ value} = \frac{14.14}{12.74} = 1.10$

vi) peak factor  $K_p = \frac{Maximum\ value}{RMS\ value} = \frac{20}{14.14} = 1.41$

instantaneous value at  $t=3\text{ms}$   $i=?$

$$i = I_m \sin \omega t$$

$$\omega = 2\pi f = 2 \times 3.14 \times 100 = 628 \text{ r/s}$$


$$\text{therefore } i = 20 \sin 628 \times 3 \times 10^{-3}$$

$$i = 0.657 \text{ A}$$

To determine the behavior of the pure resistive, pure inductive and pure capacitive circuit and to find the relationship between voltage and current
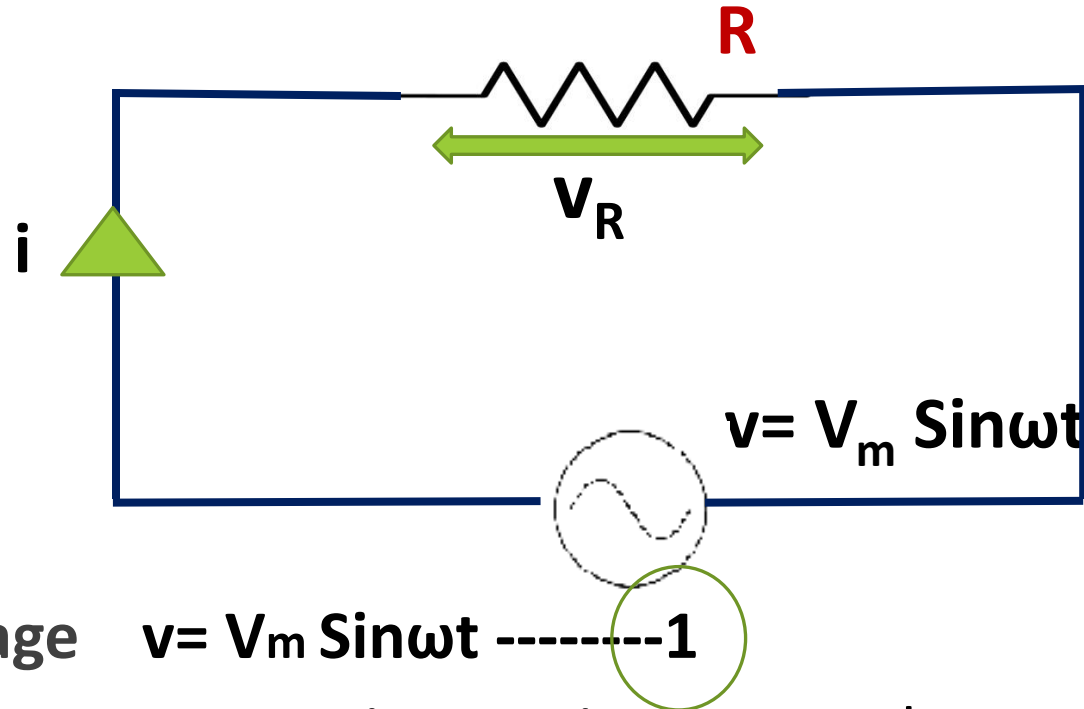
## Pure resistive circuit (R- circuit)

Consider an circuit consists of pure resistance ' $R$ '  $\Omega$  connected across an A C supply of ' $V$ ' volts.



the supply voltage  $v = V_m \sin \omega t$  -----1

Since the voltage across resistance is same as the supply voltage

$$v = v_R = iR$$

$$i = \frac{v}{R}$$

$$i = \frac{V_m \sin \omega t}{R}$$

**WKT**,  $I_m = \frac{V_m}{R}$


Therefore

$$i = I_m \sin \omega t \quad \text{--- 2}$$


Comparing equation 1 and 2

**In Pure Resistive circuit the Voltage and current are in Inphase**

## Phasor Diagram or vector diagram

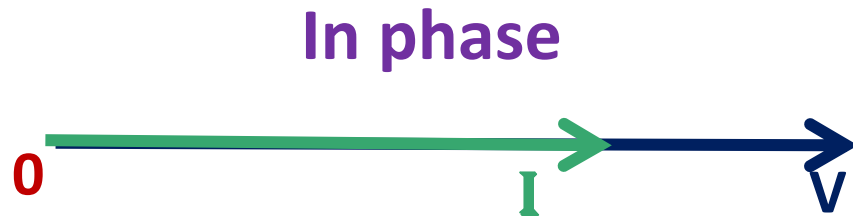

## Waveforms

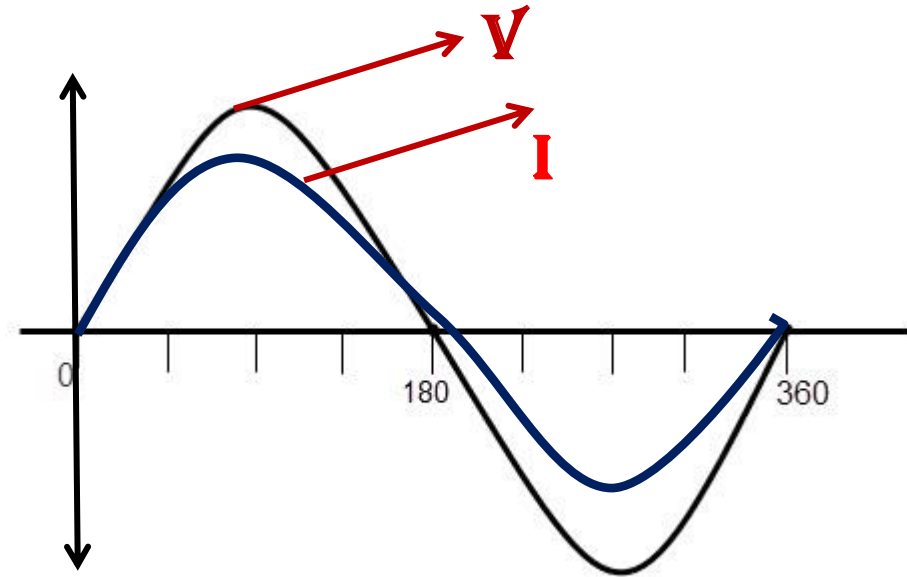

**Power Factor ( $\cos\phi$ ):** It is defined as the cosine of angle between Voltage and the current.

**For pure resistive circuit** angle between voltage and current is zero  
I,e  $\phi = 0$

Therefore  $\text{pf} = \cos\phi = \cos 0 = 1$  (unity power factor)

# Power

$$p=vi$$

$$p = V_m \sin \omega t \times I_m \sin \omega t$$

$$p = V_m I_m \sin^2 \omega t = V_m I_m \left[ \frac{1 - \cos 2\omega t}{2} \right]$$

Wkt **Average power** =  $\frac{\text{area under curve over a cycle}}{\text{length of base over a cycle}}$

$$P_{av} = \frac{\int_0^{2\pi} V_m I_m \left[ \frac{1 - \cos 2\omega t}{2} \right] d\omega t}{2\pi}$$

$$= \frac{V_m I_m}{4\pi} \int_0^{2\pi} 1 - \cos 2\omega t d\omega t$$

$$P_{av} = \frac{V_m I_m}{4\pi} \left[ \omega t - \frac{\sin 2\omega t}{2} \right]_0^{2\pi}$$

$$= \frac{V_m I_m}{4\pi} \left[ (2\pi - 0) - \frac{1}{2} (\sin 2x 2\pi - \sin 2x 0) \right]$$


$$= \frac{V_m I_m}{4\pi} \left[ (2\pi) - \frac{1}{2} (0 - 0) \right]$$

$$= \frac{V_m I_m}{4\pi} (2\pi)$$

$$P = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} = V_{rms} I_{rms}$$



## Waveforms

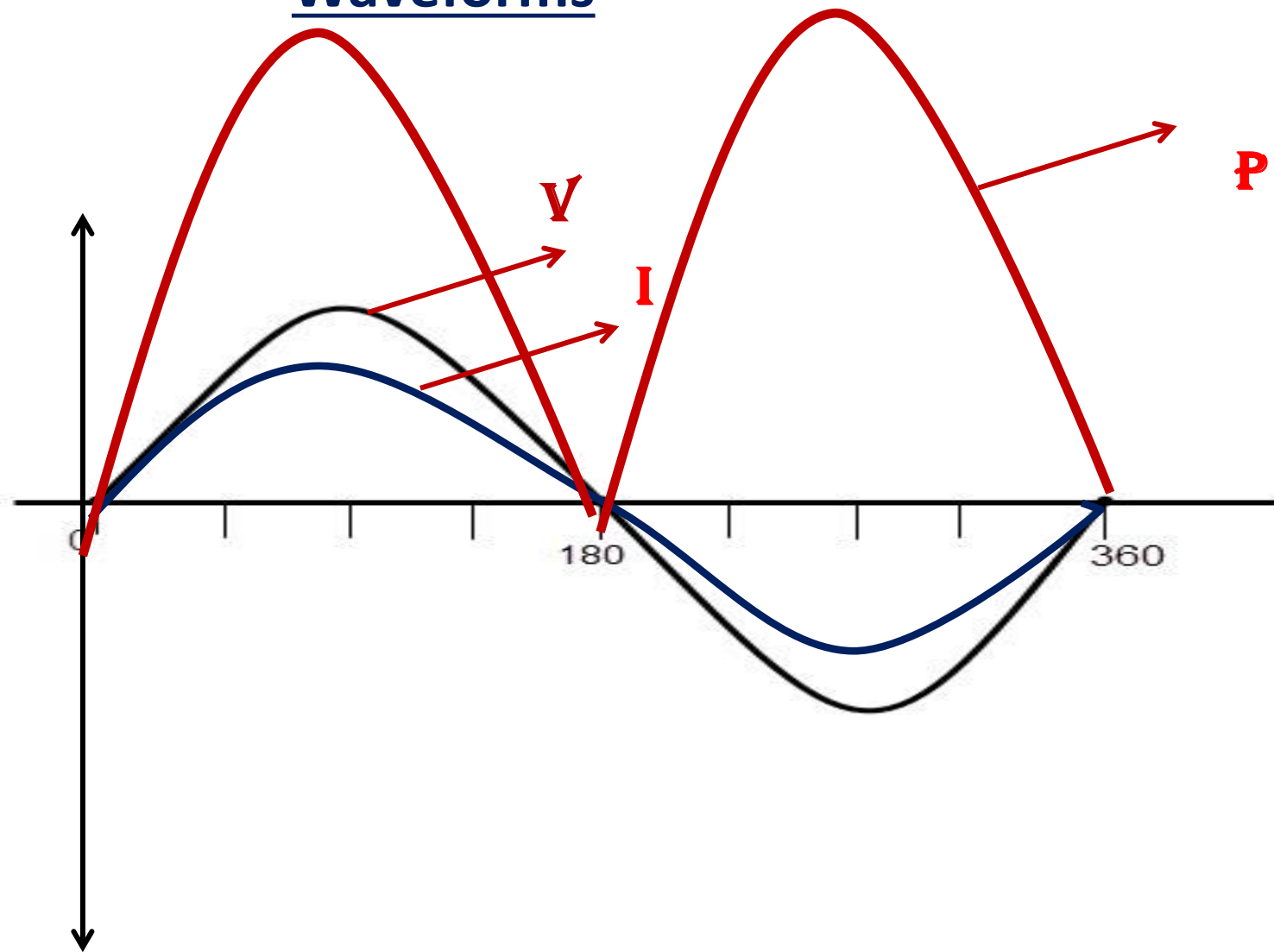

**Impedance(z)** : The total opposition offered by an AC circuit to the flow of an alternating current is called Impedance.

The unit is ohms

$$Z = V/I \quad \text{ohms}(\Omega)$$

$$Z = R \pm jX = z \angle \phi$$

**Note:** For a pure resistive circuit (R circuit)


$$Z = R + j0 = R \quad \Omega$$

$$v = V_m \sin \omega t \quad i = I_m \sin \omega t \quad \text{and} \quad P = VI$$

In polar form-  $V \angle 0$  and  $I \angle 0$
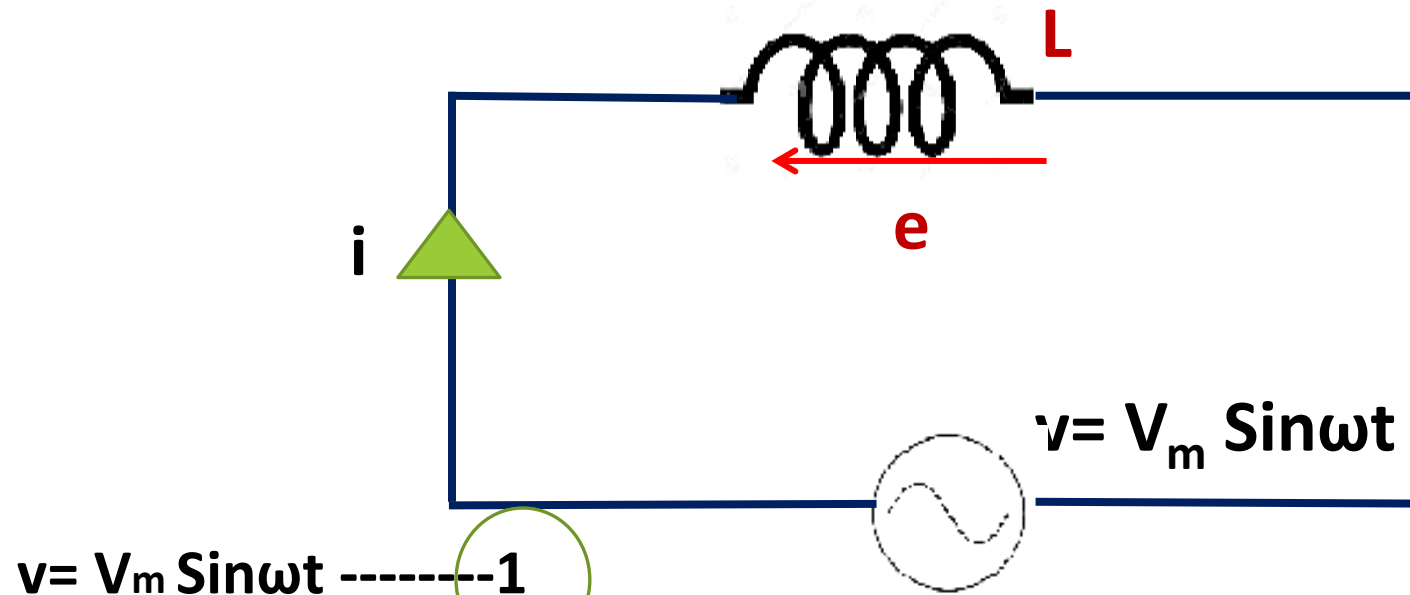
# Pure Inductive circuit (L- circuit)

Consider an circuit consists of pure Inductor of 'L' Henry connected across an A C supply of 'V' volts.



By Faraday's law

$$e = -L \frac{dI}{dt}$$

According to the Lenz's Law  **$e = -V$**

$$v = L \frac{dI}{dt}$$

$$dI = \frac{v dt}{L} = \frac{V_m \sin \omega t dt}{L}$$

Integrating both sides  $\int dI = \int \frac{V_m \sin \omega t dt}{L}$

$$i = \frac{V_m}{L} \int \sin \omega t$$

$$i = \frac{V_m}{L} \left[ \frac{-\cos \omega t}{\omega} \right]$$

$$i = \frac{V_m}{\omega L} \left[ -\sin\left(\frac{\pi}{2} - \omega t\right) \right]$$

$$i = \frac{V_m}{\omega L} \left[ \sin\left(\omega t - \frac{\pi}{2}\right) \right]$$

Wkt Inductive Reactance  $X_L = \omega L = 2\pi f L \ \Omega$

$$i = \frac{V_m \sin\left(\omega t - \frac{\pi}{2}\right)}{X_L}$$


**WKT,**  $I_m = \frac{V_m}{X_L}$

Therefore  $i = I_m \sin(\omega t - \pi/2)$ -----2


Comparing equation 1 and 2

In Pure Inductive circuit the current **lag** the voltage exactly by 90 .

Phasor diagram

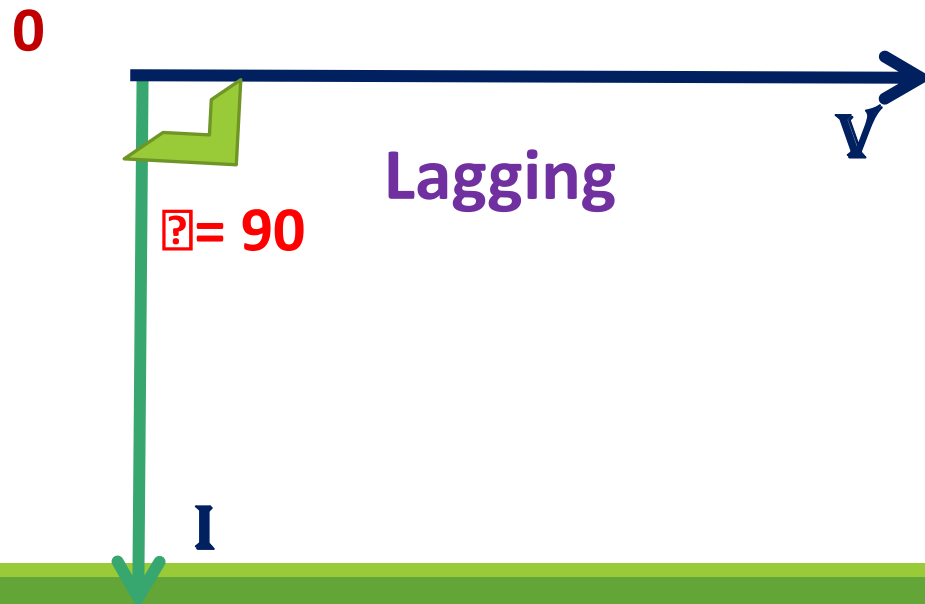

waveforms

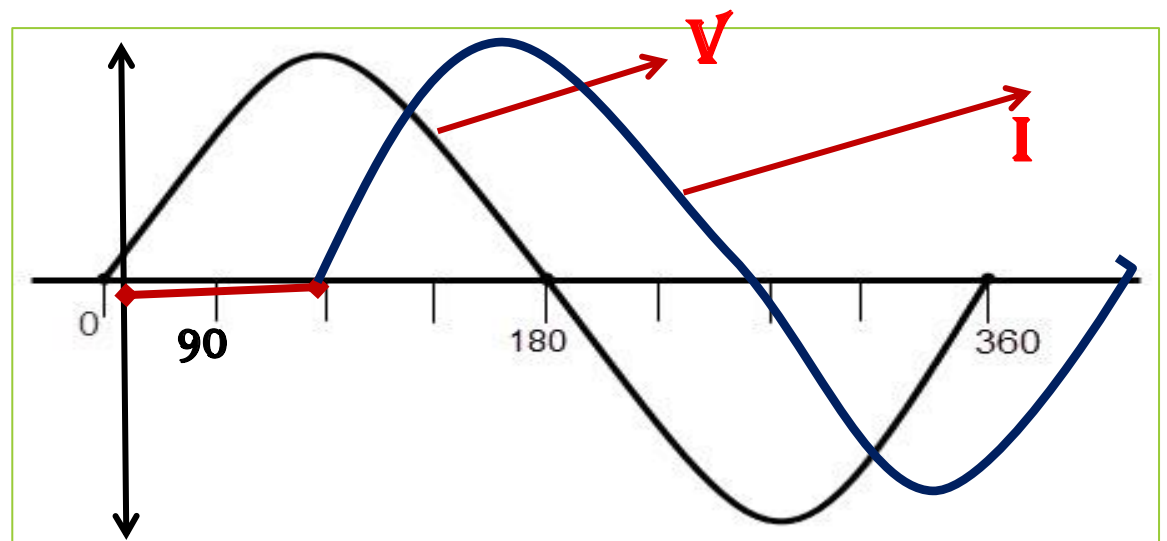

## Power of pure Inductive circuit

$$P = vi = V_m \sin \omega t \times I_m \sin(\omega t - \pi/2)$$

$$P = V_m I_m \sin \omega t (-\cos \omega t)$$

$$P = -V_m I_m \frac{\sin 2\omega t}{2}$$

As  $2 \sin \omega t \cos \omega t = \sin 2\omega t$

$$P_{av} = \int_0^{2\pi} \frac{-V_m I_m}{2} \sin 2\omega t \, d\omega t = \frac{-V_m I_m}{2} \left[ -\frac{\cos 2\omega t}{2} \right]_0^{2\pi}$$

$$P_{av} = \frac{V_m I_m}{4} [\cos 2(2\pi) - \cos(0)]$$


$$P_{av} = \frac{V_m I_m}{4} [1 - 1] = 0$$

$$P_{av} = 0$$

The average value over a cycle of the fluctuating sine component is zero.

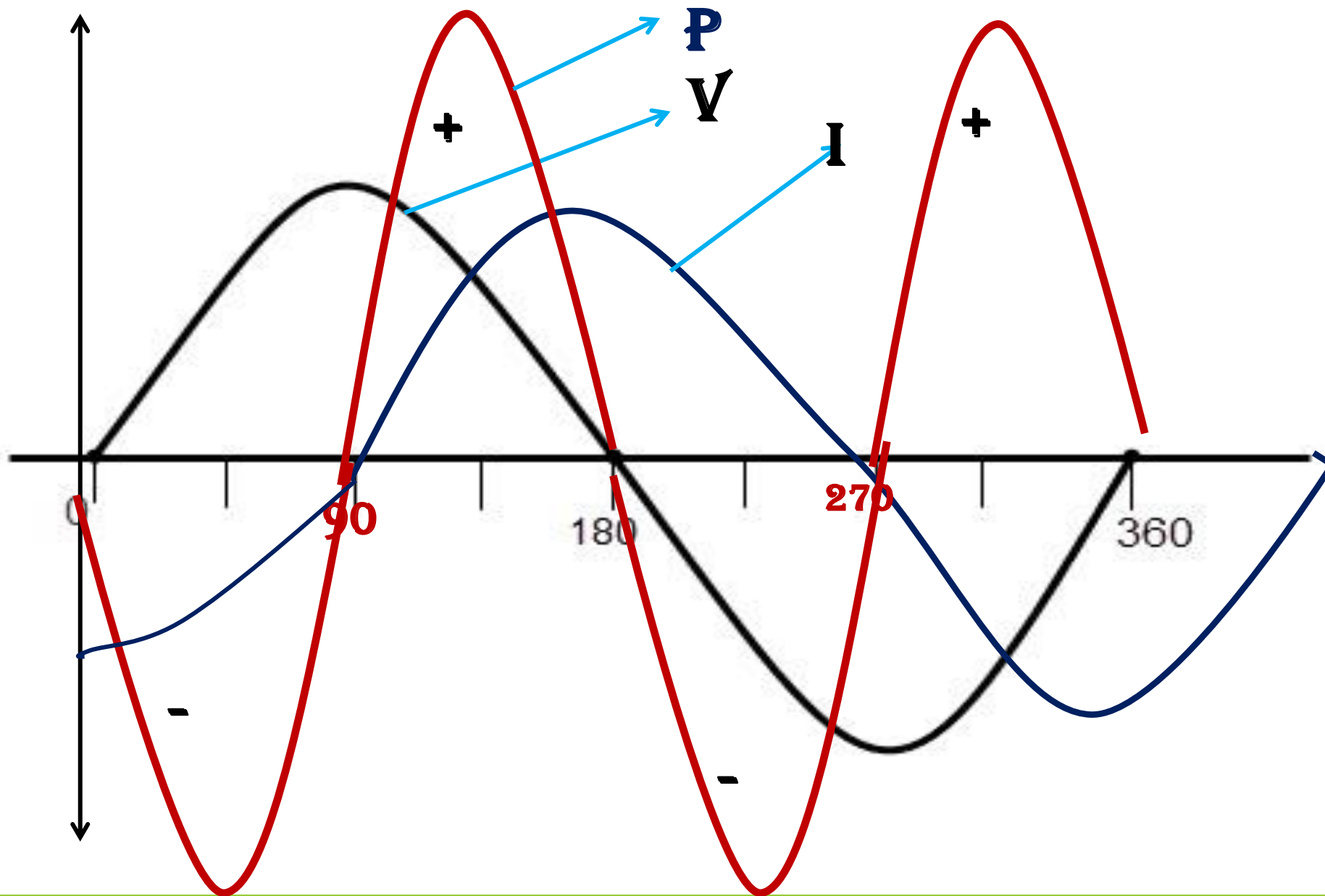So the average power consumed by an pure inductor is zero





**Note:** For a pure Inductive circuit (L circuit)

$$v = V_m \sin \omega t \quad i = I_m \sin(\omega t - \pi/2) \quad \text{and} \quad P_{av} = 0$$


In polar form  $V \angle 0$  and  $I \angle -90$

**Impedance :**

$$Z = \frac{V \angle 0}{I \angle -90} = X \angle 90 = 0 + jX_L = jX_L$$
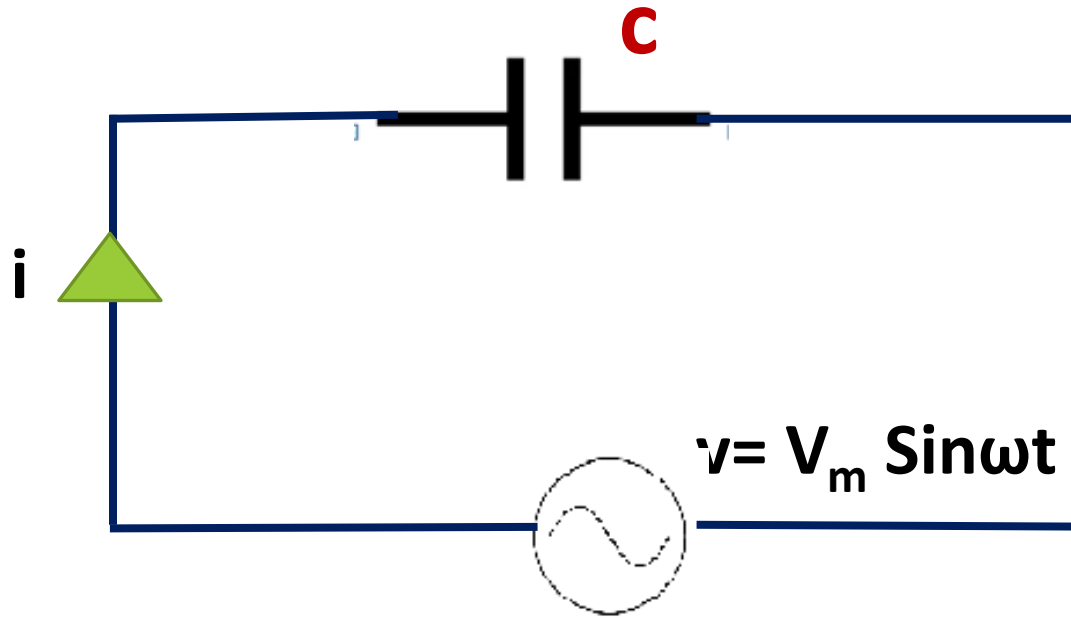
# Pure Capacitive circuit (C- circuit)

Consider an circuit consists of pure capacitor of 'C' farad's connected across an A C supply of 'V' volts.



$$v = V_m \sin \omega t \text{ -----1}$$

wkt  $q = CV$

where  $q$  = charge in coulomb's and  $C$  - capacitance of a capacitor in farad's (F)

$$q = c V_m \sin \omega t$$

differentiating both sides w.r.t 't'

$$\begin{aligned} \frac{dq}{dt} &= \frac{d(c V_m \sin \omega t)}{dt} \\ &= c V_m \frac{d(\sin \omega t)}{dt} \end{aligned}$$

wkt  $i = \frac{dq}{dt}$

Therefore,  $i = c V_m (\omega \cos \omega t)$

$$i = c \omega V_m (\cos \omega t)$$

$$i = \omega c V_m \sin (\pi/2 + \omega t)$$


$$i = \frac{V_m}{1/\omega C} \sin(\pi/2 + \omega t)$$

wkt capacitive reactance ,  $X_c = 1/\omega C = \frac{1}{2\pi f C}$

$$i = \frac{V_m}{X_c} \sin(\pi/2 + \omega t)$$

wkt ,  $I_m = \frac{V_m}{X_c}$

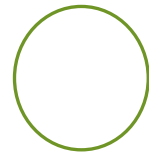
$$i = I_m \sin(\omega t + \pi/2) \text{-----2}$$




Comparing equation 1 and 2

In Pure Capacitive circuit the current **leads** the voltage exactly by 90 .

**Phasor diagram**

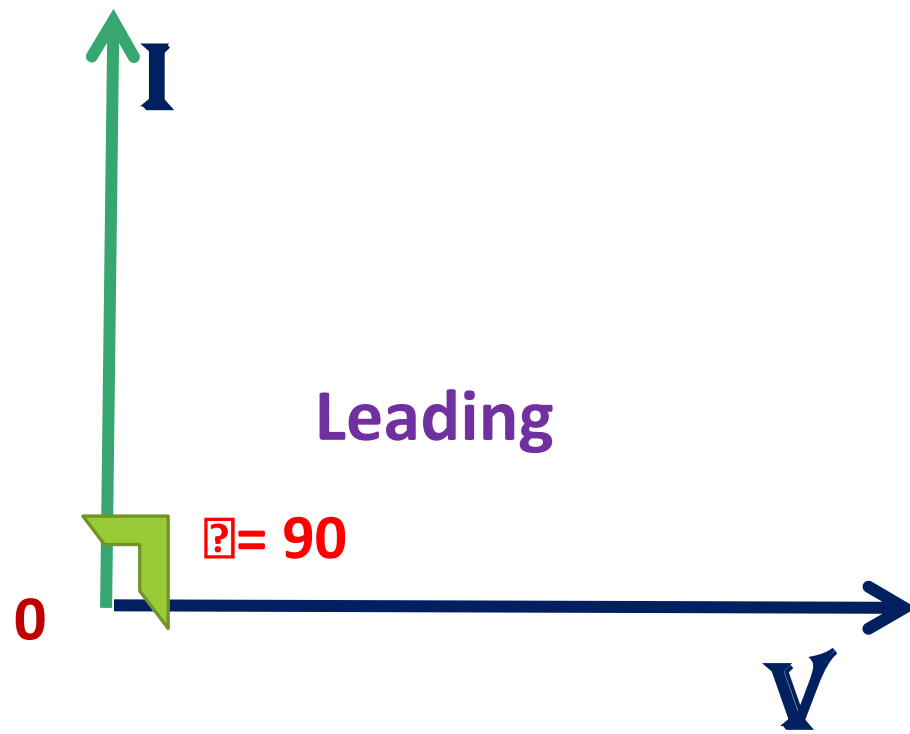

**waveforms**

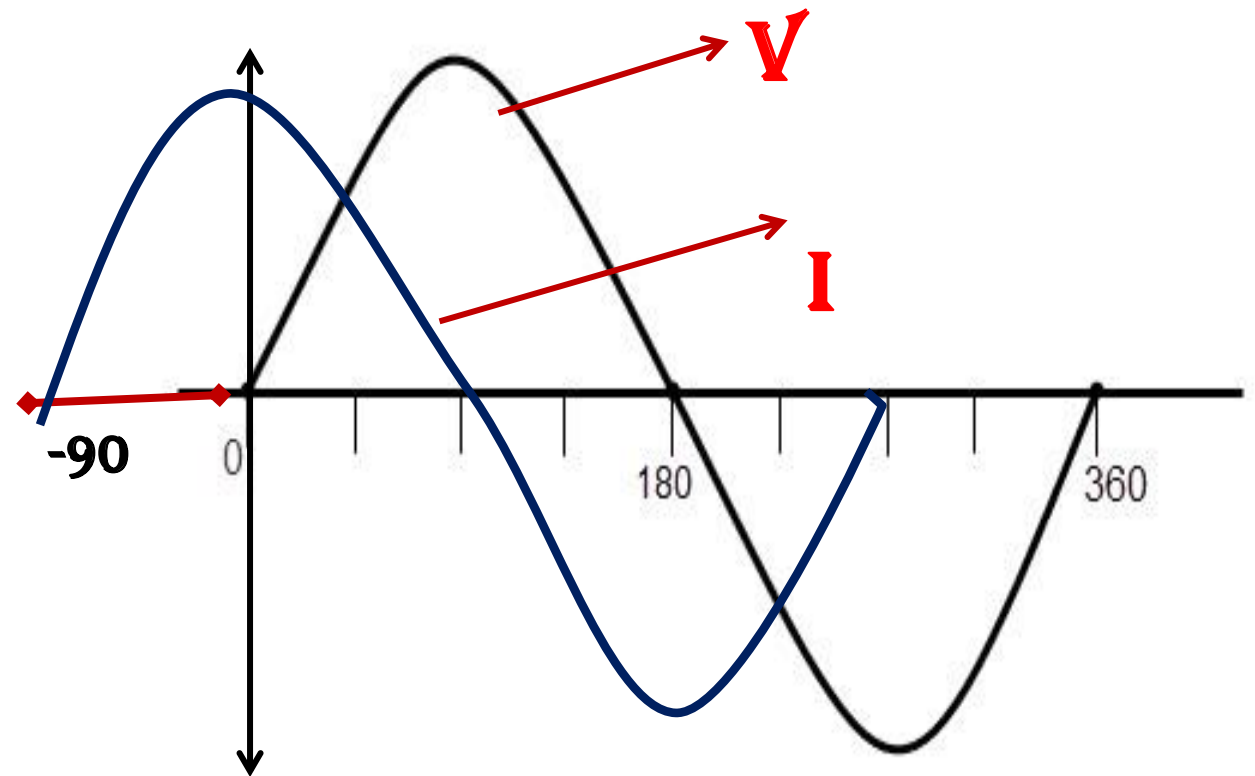

## Power of pure capacitive circuit

$$P = vi = V_m \sin \omega t \times I_m \sin(\pi/2 + \omega t)$$

$$P = V_m I_m \sin \omega t (\cos \omega t)$$

$$P = V_m I_m \frac{\sin 2\omega t}{2}$$

As  $2\sin \omega t \cos \omega t = \sin 2\omega t$

The average power consumed over a cycle

$$P_{av} = \int_0^{2\pi} \frac{V_m I_m}{2} \sin 2\omega t \, d\omega t = \frac{V_m I_m}{2} \left[ -\frac{\cos 2\omega t}{2} \right]_0^{2\pi}$$

$$P_{av} = \frac{-V_m I_m}{4} [\cos 2(2\pi) - \cos(0)]$$


$$P_{av} = \frac{-V_m I_m}{4} [1 - 1] = 0$$

$$P_{av} = 0$$

The average value over a cycle of the fluctuating sine component is zero.

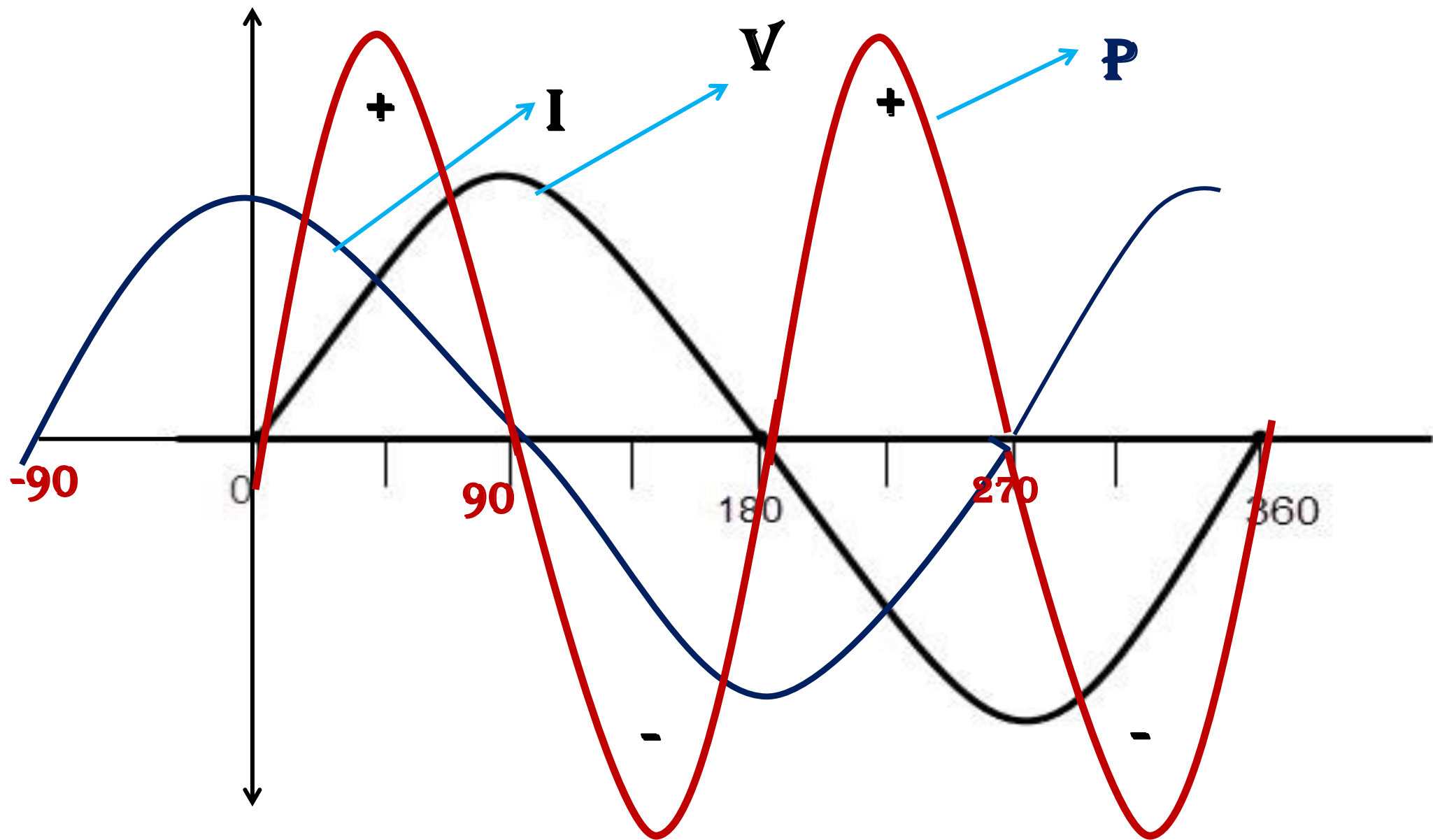So the average power consumed by an pure capacitor is zero





**Note:** For a pure capacitor circuit (C circuit)

$$v = V_m \sin \omega t \quad i = I_m \sin(\omega t + \pi/2) \quad \text{and} \quad P_{av} = 0$$

In polar form-  $V \angle 0$  and  $I \angle 90$

Impedance:  $z = R \pm jX$

$$Z = \frac{V \angle 0}{I \angle 90} = X_c \angle -90 = 0 - jX_c = -jX_c$$

# Problems on R,L, and C circuit

## Formulas

➤ **Impedance:**  $Z = \frac{V}{I}$

➤ **For pure Resistive circuit** :  $v = V_m \sin \omega t$      $i = I_m \sin \omega t$     and

$$P = V_{rms} \times I_{rms} = VI$$

In polar form-  $V \angle 0$     and     $I \angle 0$     and  $Z = R \angle 0 = R + j0$

➤ **For pure Inductive circuit** :  $v = V_m \sin \omega t$      $i = I_m \sin(\omega t - \pi/2)$

$$P_{av} = 0 \quad \mathbf{X_L = 2\pi fL} \quad \text{ohm's}$$

$$Z = X_L \angle 90 = jX_L$$

➤ **For pure capacitive circuit** :  $v = V_m \sin \omega t$      $i = I_m \sin(\omega t + \pi/2)$

$$P_{av} = 0 \quad \mathbf{X_c = 1/2\pi fc} \quad \text{ohm's}$$

$$Z = X_c \angle -90 = -jX_c$$

# Problems

1. A pure Inductor of Inductance 20mH is connected across an ac supply of 230V, 50Hz . Find the current drawn by an Inductor.

**Solution:**  $L=20 \times 10^{-3} \text{ H}$  ,  $V=230\angle 0 \text{ V}$  and  $f=50\text{Hz}$   $I=?$

$$\text{w.k.t } X_L = 2\pi fL = 2*3.142*50*20 \times 10^{-3}$$

$$Z=j X_L = j6.284 \Omega$$

$$\text{Therefore } I = \frac{V}{Z} = \frac{230\angle 0}{j6.284} = -j36.60 \text{ A} = 36.6\angle -90 \text{ A}$$

2. The current drawn by pure capacitor  $20\mu\text{F}$  is  $1.382\text{ A}$  connected across an ac supply of  $220\text{V}$ . Find the supply frequency.

Solution:  $C=20 \times 10^{-6}\text{ F}$  ,  $V=220\angle 0\text{V}$  and  $I= 1.382\text{A}$   $f=?$

w.k.t for pure capacitor circuit

$$Z=-jX_c = \frac{V}{I} = \frac{220\angle 0}{1.382}$$

$$X_c = 159.18\Omega$$

$$\text{Therefore } X_c = \frac{1}{2\pi f C}$$

$$f = \frac{1}{2\pi C X_c} = \frac{1}{2 \times 3.142 \times 159.18 \times 20 \times 10^{-6}} = 49.99 = 50\text{Hz}$$

3. The current drawn by pure Inductor of 30H is 2A. connected across an ac supply of 220V. Find the supply frequency.

**Solution** :  $L = 30$  ,  $I = 2$  A  $V = 220$   $f = ?$

$$Z = jX_L = V/I = 220/2 = 110\Omega \quad \text{and}$$

$$X_L = 2\pi f L$$

$$110 = 2\pi f \cdot 30$$

$$f = 0.58\text{Hz} \approx 1\text{Hz}$$

4. A pure capacitor of 50F is connected to a Ac source of 230V,50Hz .find current drawn by the circuit and also capacitive reactance.

**Solution:**  $c = 50$   $V = 230$  v  $f = 50$ Hz  $I = ?$   $X_c = ?$

$$X_c = 1 / (2 \pi f C) = 6.3 \times 10^{-5} \Omega$$

$$Z = -jX_c = -j 6.3 \times 10^{-5}$$

$$I = V / Z = 230 / -j 6.3 \times 10^{-5} = j 3.6 \times 10^6 \text{ A}$$

4. A pure capacitor of 50F is connected to a Ac source of 230V,50Hz .find current drawn by the circuit and also capacitive reactance.

**Solution:**  $c = 50$   $V = 230$  v  $f = 50\text{Hz}$   $I = ?$   $X_c = ?$

$$X_c = 1 / (2 \times 3.142 \times f \times C) = 6.3 \times 10^{-5} \Omega$$


$$Z = -jX_c = -j 6.3 \times 10^{-5}$$

$$I = V / Z = 230 / -j 6.3 \times 10^{-5} = j 3.6 \times 10^6 \text{ A}$$


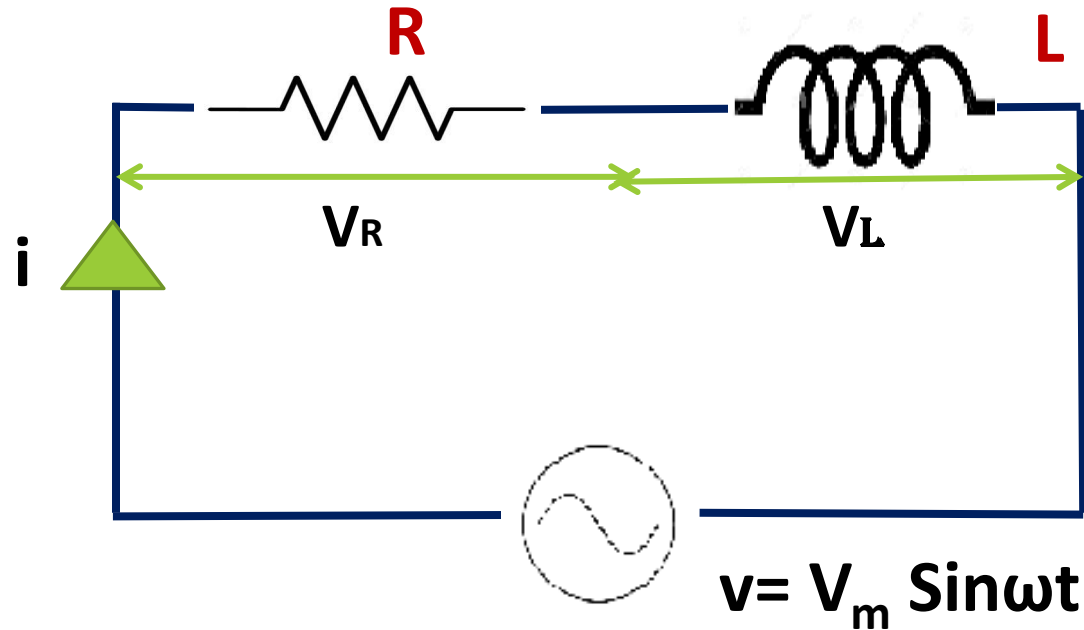
# R-L Circuit

Consider an circuit of resistance ' $R$ '  $\Omega$  connected in series with an Inductor of ' $L$ ' Henry across an A C supply of ' $V$ ' volts.



$$v = V_m \sin \omega t \text{ -----1}$$


$V_R$  = Voltage drop across ' $R$ ' and  $V_L$  = Voltage drop across ' $L$ '

$$V_R = IR$$

$$V_L = IX_L, \text{ where } X_L = 2\pi fL \ \Omega$$

The vector sum

$$\bar{V} = \bar{V}_R + \bar{V}_L$$

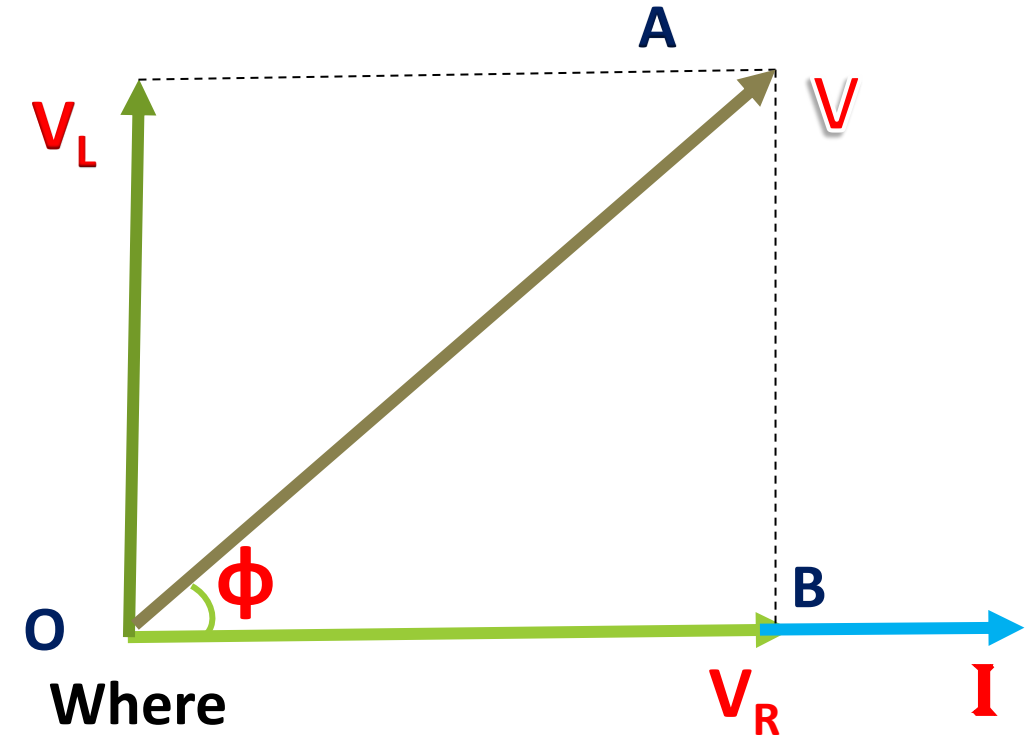

Where


$V_R$  is in phase with current

$V_L$  leads current by angle of 90


phasor diagram

$$i = I_m \sin(\omega t - \phi) \text{----- } 2$$

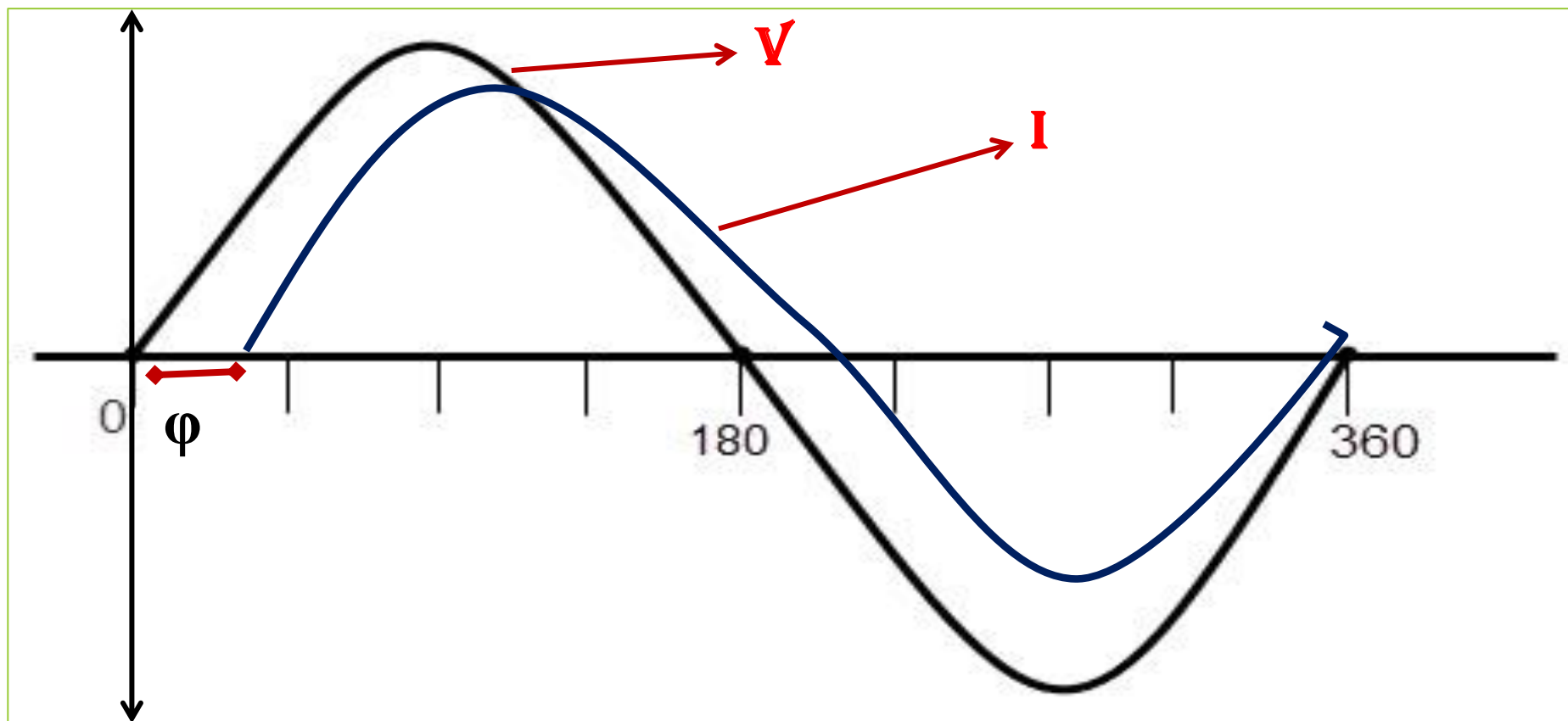by comparing equation 1 and 2 in R-L the current lags the voltage by an of  $\phi$



Considering a triangle OAB

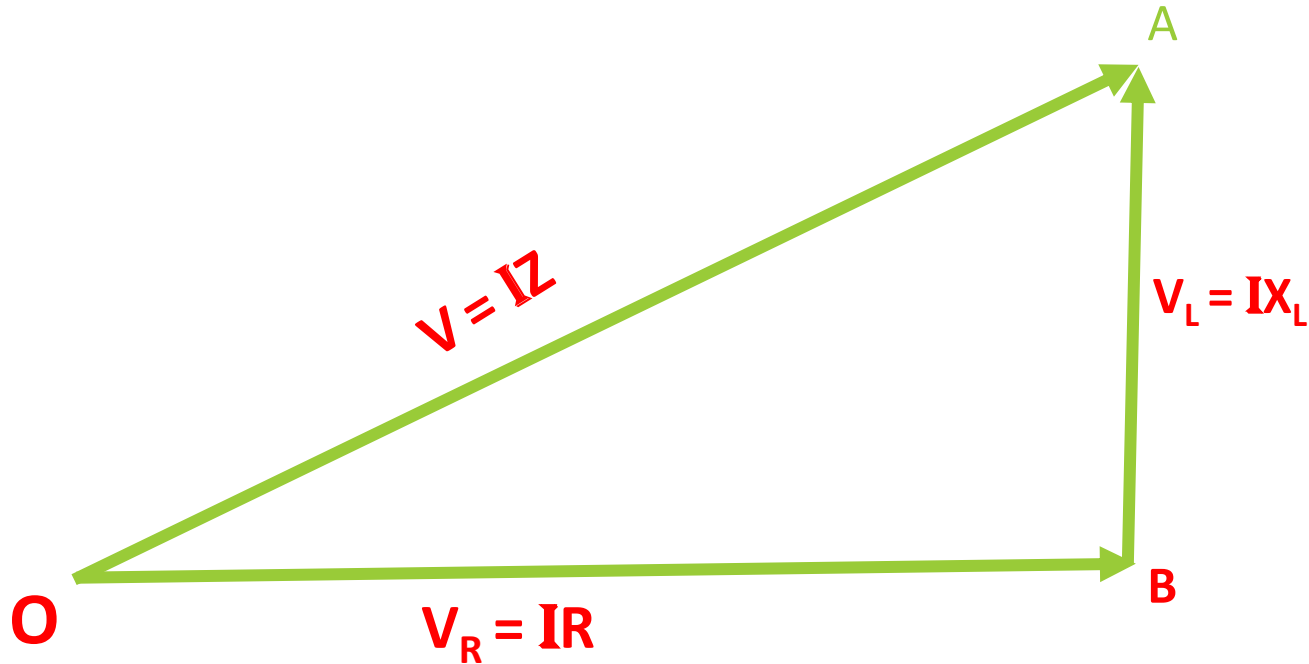


$$V = \sqrt{V_R^2 + V_L^2}$$

$$V = \sqrt{(IR)^2 + (IX_L)^2}$$

$$V = I\sqrt{R^2 + X_L^2}$$

Where  $\sqrt{R^2 + X_L^2} = Z$ , impedance of the circuit

# Impedance Triangle

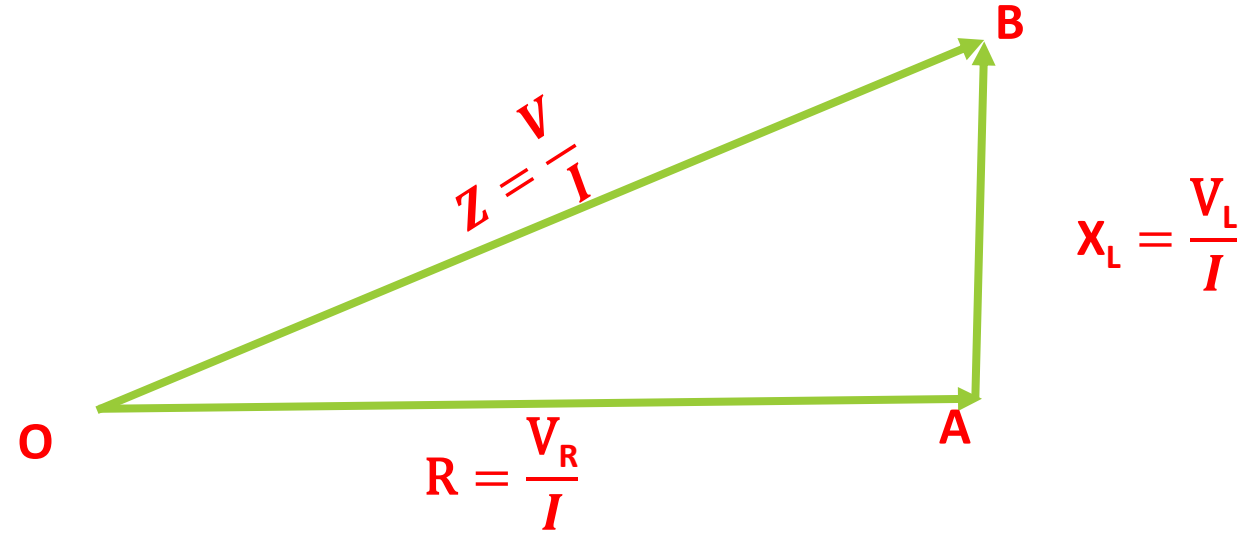

$$Z = R + jX_L \quad \Omega = \sqrt{R^2 + X_L^2}$$

Power factor  $\cos \phi = \frac{R}{Z}$

## Power of R-L circuit

Instantaneous power  $\mathbf{p=vi}$

$$=V_m \sin \omega t \times I_m \sin(\omega t - \varphi)$$

$$P = V_m I_m \sin \omega t \sin(\omega t - \varphi)$$

$$\sin A \sin B = \frac{\cos(A-B)}{2} - \frac{\cos(A+B)}{2}$$

$$P = V_m I_m \left[ \frac{\cos(\omega t - (\omega t - \varphi))}{2} - \frac{\cos(\omega t + (\omega t - \varphi))}{2} \right]$$

$$P = \frac{V_m I_m}{2} [\cos(\omega t - \omega t + \varphi) - \cos(\omega t + \omega t - \varphi)]$$

$$P = \frac{V_m I_m}{2} [\cos(\varphi) - \cos(2\omega t - \varphi)]$$

The average power consumed over a cycle

$$P_{av} = \frac{\int_0^{2\pi} \frac{V_m I_m}{2} [\cos(\varphi) - \cos(2\omega t - \varphi)] d\omega t}{2\pi}$$

$$P_{av} = \frac{V_m I_m}{4\pi} \left[ \int_0^{2\pi} \cos\varphi \, d\omega t - \int_0^{2\pi} \cos(2\omega t - \varphi) \, d\omega t \right]$$

{ the average value of  $\cos(2\omega t - \varphi) = 0$  }.

$$P_{av} = \frac{V_m I_m \cos\varphi}{4\pi} [\omega t]_0^{2\pi} = \frac{V_m I_m \cos\varphi}{4\pi} [2\pi - 0]$$


$$P_{av} = \frac{V_m I_m \cos\varphi}{4\pi} [2\pi] = \frac{V_m I_m \cos\varphi}{2}$$

$$P_{av} = \frac{V_m I_m \cos\varphi}{\sqrt{2} \sqrt{2}} = V_{rms} I_{rms} \cos\varphi$$

$$P = V I \cos\varphi$$
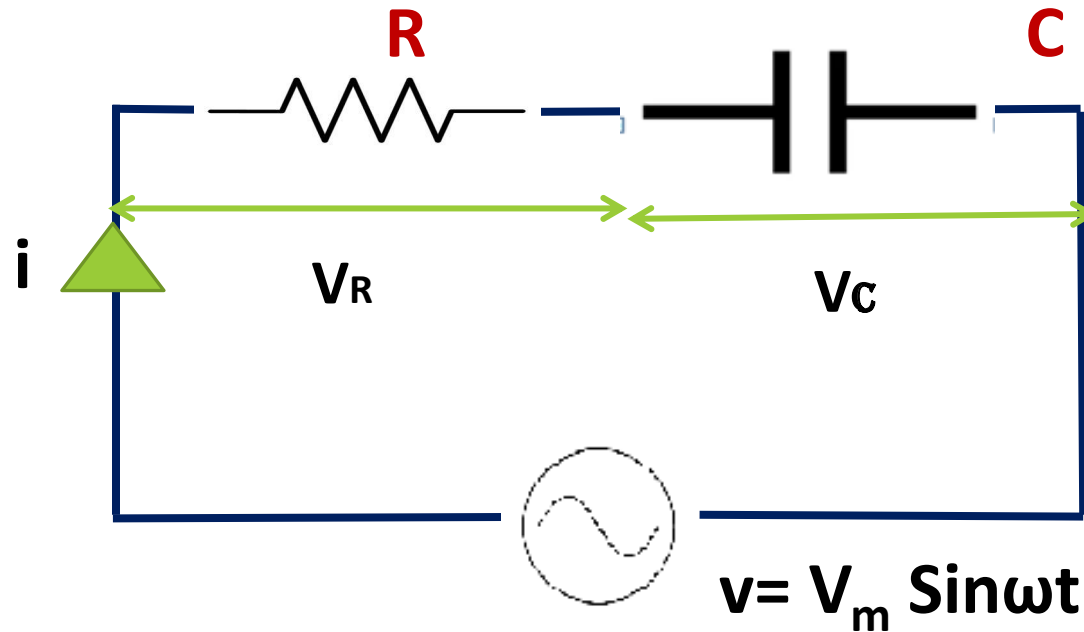
# R-C Circuit

Consider an circuit of resistance ' $R$ '  $\Omega$  connected in series with an Capacitor of ' $C$ ' Farads across an A C supply of ' $V$ ' volts.



$$V = V_m \sin \omega t \text{ -----1}$$

$V_R$  = Voltage drop across ' $R$ ' and  $V_C$  = Voltage drop across ' $C$ '



$$V_R = IR$$

$$V_c = IX_c$$

$$\text{where } X_c = 1/2\pi f c \Omega$$


The vector sum

$$\bar{V} = \bar{V}_R + \bar{V}_c$$

Phasor diagram

$$i = I_m \sin(\omega t + \phi) \text{----- } 2$$

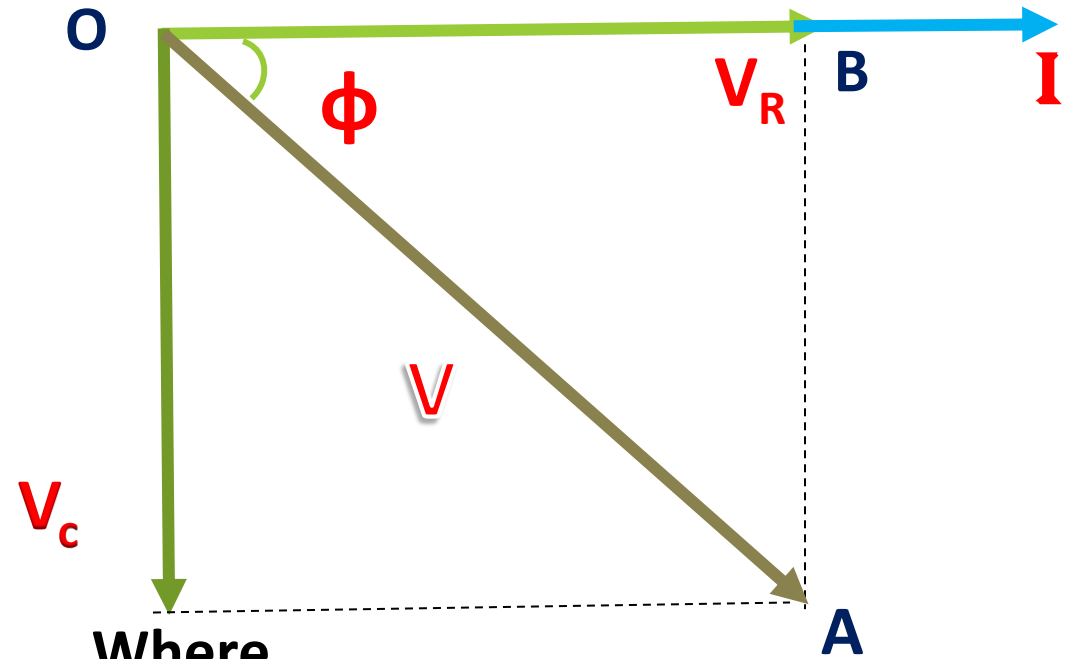
by comparing equation 1 and 2 in R-C the current leads the voltage by an of  $\phi$




Where

$V_R$  is in phase with current

$V_c$  lags current by angle of 90

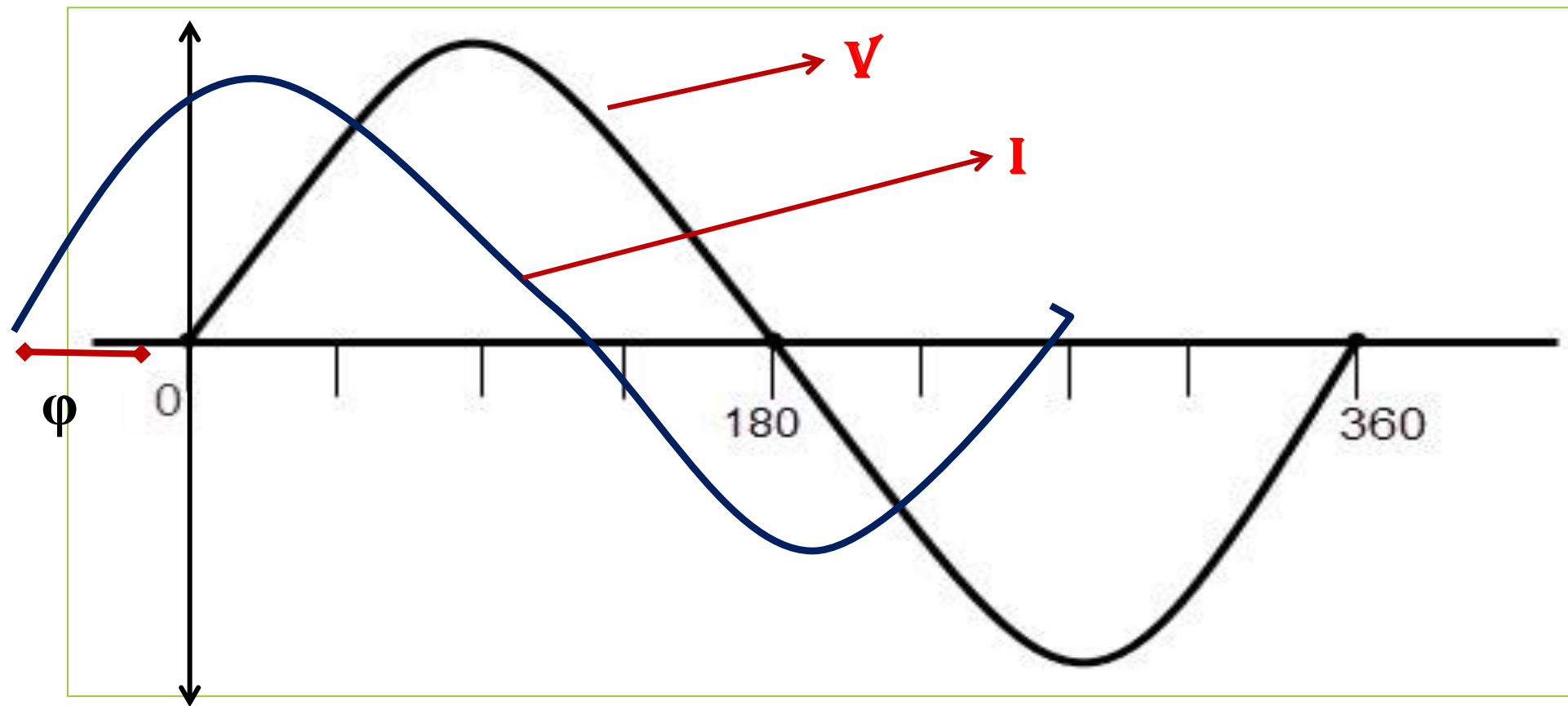

Considering a triangle OAB

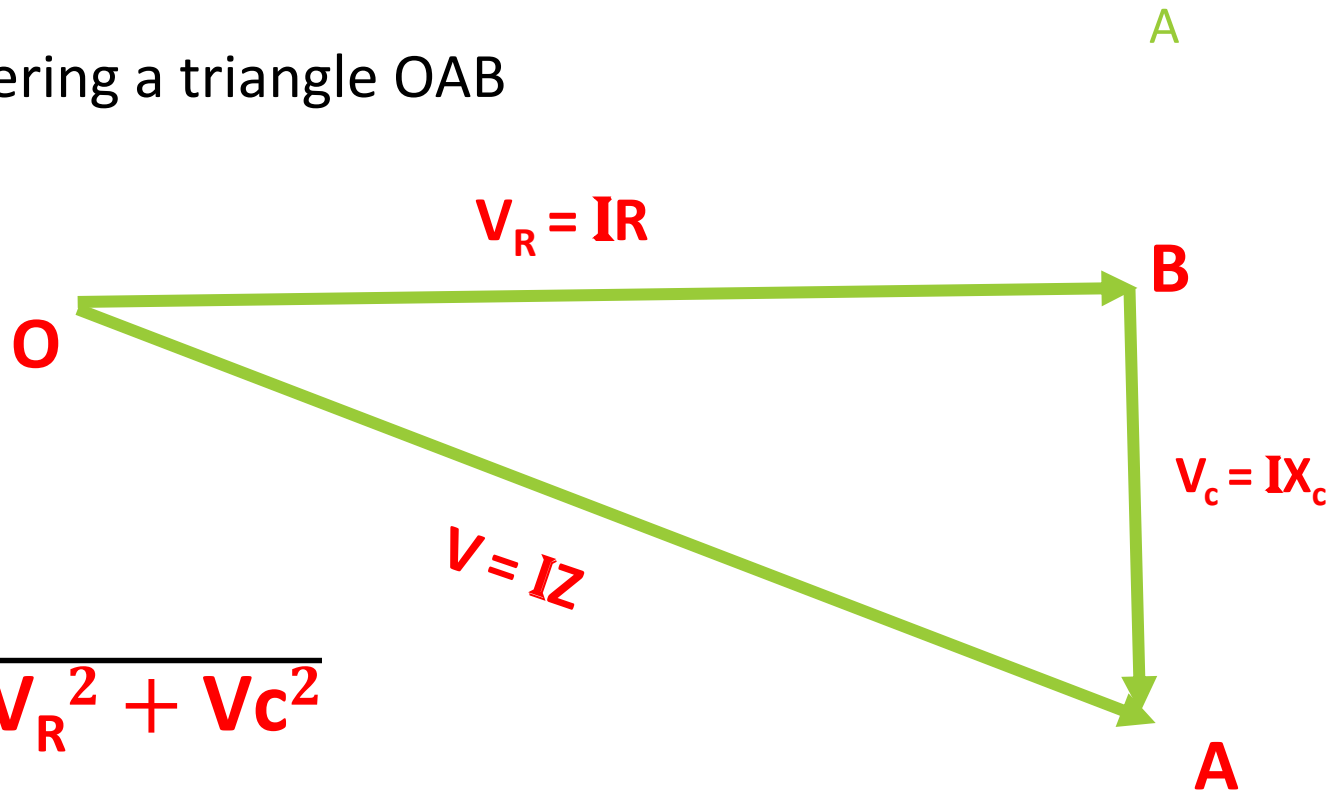

$$V = \sqrt{V_R^2 + V_c^2}$$

$$V = \sqrt{(IR)^2 + (IX_c)^2}$$

$$V = I\sqrt{R^2 + X_c^2}$$


Where  $\sqrt{R^2 + X_c^2} = Z$ , impedance of the circuit

# Impedance triangle

$$Z = R - jX_c \quad \Omega = \sqrt{R^2 + X_c^2}$$

$$Z = \frac{V \angle 0}{I \angle \phi} = Z \angle -\phi$$
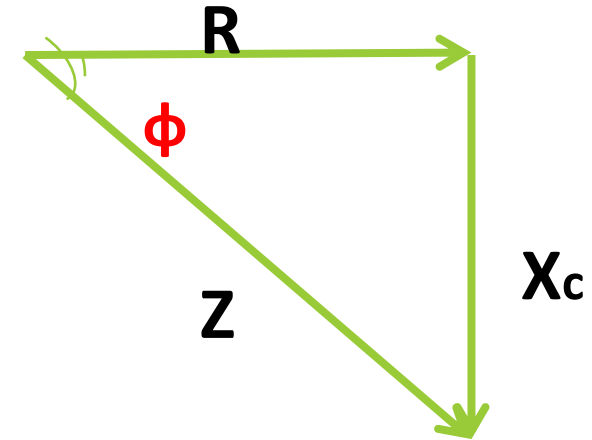
$$\text{Power factor} \quad \cos \phi = \frac{R}{Z}$$



## Power of circuit

Instantaneous power  $\mathbf{p=vi}$

$$=V_m \sin \omega t \times I_m \sin(\omega t + \varphi)$$

$$P = V_m I_m \sin \omega t \sin(\omega t + \varphi) \quad \sin A \sin B = \frac{\cos(A-B)}{2} - \frac{\cos(A+B)}{2}$$

$$P = V_m I_m \left[ \frac{\cos(\omega t - (\omega t + \varphi))}{2} - \frac{\cos(\omega t + (\omega t + \varphi))}{2} \right]$$

$$P = \frac{V_m I_m}{2} [\cos(\omega t - \omega t - \varphi) - \cos(\omega t + \omega t + \varphi)]$$

$$P = \frac{V_m I_m}{2} [\cos(-\varphi) - \cos(2\omega t + \varphi)]$$

The average power consumed over a cycle

$$P_{av} = \frac{\int_0^{2\pi} \frac{V_m I_m}{2} [\cos(\varphi) - \cos(2\omega t + \varphi)] d\omega t}{2\pi}$$

$$P_{av} = \frac{V_m I_m}{4\pi} \left[ \int_0^{2\pi} \cos\varphi \, d\omega t - \int_0^{2\pi} \cos(2\omega t + \varphi) \, d\omega t \right]$$

{ the average value of  $\cos(2\omega t - \phi)$  = 0 }.

$$P_{av} = \frac{V_m I_m \cos\varphi}{4\pi} [\omega t]_0^{2\pi} = \frac{V_m I_m \cos\varphi}{4\pi} [2\pi - 0]$$

$$P_{av} = \frac{V_m I_m \cos\varphi}{4\pi} [2\pi] = \frac{V_m I_m \cos\varphi}{2}$$

$$P_{av} = \frac{V_m I_m \cos\varphi}{\sqrt{2} \sqrt{2}} = V_{rms} I_{rms} \cos\varphi$$

$$P = V I \cos\varphi$$

## Power factor (pf):

It is defined as the cosine of angle between applied voltage and current. I.e  $\cos\phi$

**where  $\phi$  – is the angle between applied voltage and current**

Significance :-

- 1) The Power factor gives the nature of the circuit by which we can decide whether it is resistive capacitive or inductive
- 2) The nature of the Power factor is always determined by the position of current w.r.t to Voltage
- 3) The Power factor varies between zero to one.

# Power

**Real or True or Active power(P)**: It is defined as the product of applied voltage an active component of the current and the unit is **Watts(W)**

$$P = V I \cos\phi \text{ watts}$$

**Apparent Power (S)**: It is defined as the product of RMS value of voltage and current and unit is **VA(volt ampere)**

$$S = V I \text{ VA}$$

**Reactive power(Q)**: It is defined as the product of applied voltage an reactive component of the current and the unit is **VAR(Volt ampere reactive)**

$$Q = V I \sin\phi \text{ VAR}$$



# Formulas of R-L and R- C circuit

$$V = \frac{V_m}{\sqrt{2}} \quad I = \frac{I_m}{\sqrt{2}} \quad \omega = 2\pi f$$

R-L circuit (current lags voltage by an angle of  $\phi$ )

$$V = V_m \sin \omega t \text{ and } I = I_m \sin(\omega t - \phi)$$

$$Z = R + jX_L \quad \Omega = \sqrt{R^2 + X_L^2}$$

R-C circuit (current leads voltage by an angle of  $\phi$ )

$$V = V_m \sin \omega t \text{ and } I = I_m \sin(\omega t + \phi)$$

$$Z = R - jX_C \quad \Omega = \sqrt{R^2 + X_C^2}$$

$$\text{Power factor} \quad \cos \phi = \frac{R}{Z}$$

Active power  $P = V I \cos\phi$  watts

Apparent power  $S = V I$  VA

Reactive power  $Q = V I \sin\phi$  VAR

1. A circuit consists of resistance of  $20\Omega$  and an Inductance of  $50\text{mH}$  is connected in series across the supply of  $250\text{V}$ ,  $50\text{Hz}$ . Determine the current, power consumed by the circuit and power factor of the circuit.

Given :  $R = 20\Omega$  ,  $L = 50\text{mH} = 50 \times 10^{-3}$  and  $V = 250\angle 0$   $f = 50\text{Hz}$

$I = ?$   $P = ?$   $\text{Pf} = ?$

Wkt The Impedance of R – L circuit is

$$Z = R + jX_L$$

Therefore  $X_L = 2\pi fL = 2 * 3.142 * 50 * 50 \times 10^{-3} = 15.7\Omega$

$$Z = R + jX_L = 20 + j15.7 \Omega = 25.42 \angle 38.18$$

$$\underline{I} = \frac{V}{Z} = \frac{250 \angle 0^\circ}{25.42 \angle 38.18^\circ} = 9.83 \angle 0 - 38.18$$

$$\boxed{\underline{I} = 9.83 \angle -38.18^\circ \text{ A}} \quad (-ve \text{ indicates lagging})$$

The current lags the voltage by an angle of

$$\Phi = \text{voltage angle} - \text{current angle} = 0 - (-38.18) = 38.18$$

$$\text{Pf} = \cos \phi = \cos(38.18^\circ) = 0.78 \text{ lagging}$$

$$P = VI \cos \phi = 250 \times 9.83 \times 0.78 = 1916.85 \text{ W}$$

Q. A non-inductive resistor of  $10\Omega$  is in series with  $100\mu\text{F}$  capacitor across  $250\text{V}$   $50\text{Hz}$  AC circuit. Determine the current taken by the capacitor & Power factor of the circuit

Given:-

$$R = 10\Omega$$
$$C = 100\mu\text{F} = 100 \times 10^{-6} \text{ F}$$
$$V = 250\text{V}$$
$$f = 50\text{Hz}$$
$$I = ?$$
$$P = ?$$

The circuit elements are  $R$  &  $C$

$$Z = R - jX_c$$

$$X_c = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.142 \times 50 \times 100 \times 10^{-6}}$$

$$Z = 10 - j 31.18$$
$$= 33.37 \angle -72.56^\circ$$

$$X_c = 31.18 \Omega$$

$$I = \frac{V}{Z} = \frac{250 \angle 0}{33.37 \angle -72.56} = 7.49 \angle (0 - (-72.56))$$

$$I = 7.49 \angle 72.56 \text{ A}$$

The current is leading by an angle of  $\phi = (0 - 72.56) = -72.56$

$$\cos \phi = \cos 72.56 = 0.3 \text{ leading}$$

$$P = VI \cos \phi = 250 \times 7.49 \times 0.3 = 561.8 \text{ W}$$

**3.The Alternating Voltage of  $V=160+j120$  V is applied to a circuit and the current is given by  $I=6-j2$  A .Find the values of circuit elements assuming supply frequency as 50Hz and also determine the Power factor**

Solution : Given  $V= 160+j120$  V     $I = 6-j2$  A

$Z=?$  ,  $f=50\text{Hz}$  And  $\cos\phi=?$

$$V=160+j120 = 200\angle 36.85^\circ \text{ V}$$

$$I=6-j2 = 6.32\angle -18.43^\circ \text{ A} \quad (\text{'-' negative signs indicates lagging})$$

The current lags the voltage by an angle of

$$\Phi = 36.86 - (-18.43) = 55.29$$

Therefore this the R-L circuit

$$Z = \frac{V}{I} = \frac{200 \angle 36.85}{6.32 \angle -18.43} = 31.64 \angle 55.29 = 18 + j26 \, \Omega$$

$$Z = 18 + j26 \, \Omega = R + jX_L$$

The circuit elements are R and L

$$R = 18 \, \Omega \text{ and } X_L = 26 \, \Omega$$

$$X_L = 2\pi f L$$

$$L = \frac{X_L}{2\pi f} = \frac{26}{2 * 3.142 * 50} = 0.082 \, \text{H}$$

$$\text{Power factor pf} = \cos\phi = \cos(55.29) = 0.56 \quad \text{Lagging}$$



**2.The Alternating Voltage of  $V=160+j120$  V is applied to a circuit and the current  $I=6+j8$  A drawn from the supply .Find the values of circuit elements assuming supply frequency as 50Hz and also determine the Power consumed**

Solution : Given  $V= 160+j120$  V     $I = 6+j8$  A

$Z=?$  ,  $f=50\text{Hz}$  And  $P =?$

$$V=160+j120 = 200\angle 36.85^\circ \text{ V}$$

$$I =6+ j8 = 10\angle 53.13^\circ \text{ A} \quad \text{('+' positive signs indicates leading )}$$

The current leads the voltage by an angle of

$$\Phi = 36.85 - 53.13 = -16.27$$

Therefore this the R-c circuit

$$Z = \frac{V}{I} = \frac{200 \angle 36.85}{10 \angle 53.13} = 20 \angle -16.27 = 19.9 - j 5.6 \Omega$$

$$Z = 19.9 - j 5.6 \Omega = R - j X_c$$

The circuit elements are R and C

$$R = 19.9 \Omega \quad \text{and} \quad X_c = 5.6 \Omega$$

$$X_c = 1 / 2\pi f C$$

$$C = \frac{1}{2\pi f X_c} = \frac{1}{2 * 3.142 * 50 * 5.6} = 0.56 \text{ mF}$$

$$\text{Power factor pf} = \cos \phi = \cos(16.27) = 0.95 \quad \text{Leading}$$

$$P = V I \cos \phi = 200 \times 10 \times \cos(16.27) = 1919.90 \text{ Watts}$$

5. Given  $V = 200 \sin 377t$  volts and  $I = 8 \sin (377t - 30^\circ)$  A for an AC circuit determine :i) frequency ii) power factor iii) True power iv) Apparent power v) Reactive power.

Given :  $V = 200 \sin 377t$  volts     $I = 8 \sin (377t - 30^\circ)$

From above equation  $V = V_m \sin \omega t$        $I = I_m \sin(\omega t - \phi)$

$V_m = 200 \text{ V}$ ,  $I_m = 8$  and  $\omega = 2\pi f = 377$

$$f = \frac{377}{2\pi} = \frac{377}{2 \times 3.142} = 60 \text{ Hz}$$

$\phi$  is an angle between voltage and current

Therefore  $\phi = 0 - (-30) = 30^\circ$

$\text{Pf} = \cos \phi = \cos(30) = 0.866$  lagging

$$V_m = 200 \text{ V}, \quad I_m = 8 \text{ A}$$

$$V = \frac{V_m}{\sqrt{2}} = \frac{200}{\sqrt{2}} = 141.42 \text{ V}$$

$$I = \frac{I_m}{\sqrt{2}} = \frac{8}{\sqrt{2}} = 5.656 \text{ A}$$

$$\text{True power } P = V I \cos\phi = 141.42 * 5.656 * \cos(30) = 692.8 \text{ Watts}$$

$$\text{Apperent power } S = VI = 141.42 * 5.656 = 800 \text{ VA}$$

$$\text{Reactive Power } Q = V I \sin\phi = 141.42 * 5.656 * \sin(30) = 400 \text{ VAR}$$

6. Given  $V = 200 \sin(377t - 30)$  volts and  $I = 8 \sin(377t + 90)$  A for an AC circuit determine : i) frequency ii) power factor iii) True power iv) Apparent power v) Reactive power

Given :  $V = 200 \sin(377t - 30)$  volts     $I = 8 \sin(377t + 90^\circ)$

From above equation  $V = V_m \sin(\omega t - \phi)$      $I = I_m \sin(\omega t + \phi)$

$V_m = 200 \text{ V}$  ,     $I_m = 8$      $\omega = 2\pi f = 377$

$$f = \frac{377}{2\pi} = \frac{377}{2 \times 3.142} = 60 \text{ Hz}$$

$\phi$  is an angle between voltage and current

Therefore  $\phi = -30 - 90 = -120^\circ$

$\text{Pf} = \cos \phi = \cos(120) = 0.5 \text{ leading}$

$$V_m = 200 \text{ V}, \quad I_m = 8 \text{ A}$$

$$V = \frac{V_m}{\sqrt{2}} = \frac{200}{\sqrt{2}} = 141.42$$

$$I = \frac{I_m}{\sqrt{2}} = \frac{8}{\sqrt{2}} = 5.656$$


$$\text{True power } P = V I \cos\phi = 141.42 * 5.656 * \cos(120) = 399.9 \text{ Watts}$$

$$\text{Apperent power } S = VI = 141.42 * 5.656 = 800 \text{ VA}$$

$$\text{Reactive Power } Q = V I \sin\phi = 141.42 * 5.656 * \sin(120) = 692.70 \text{ VAR}$$
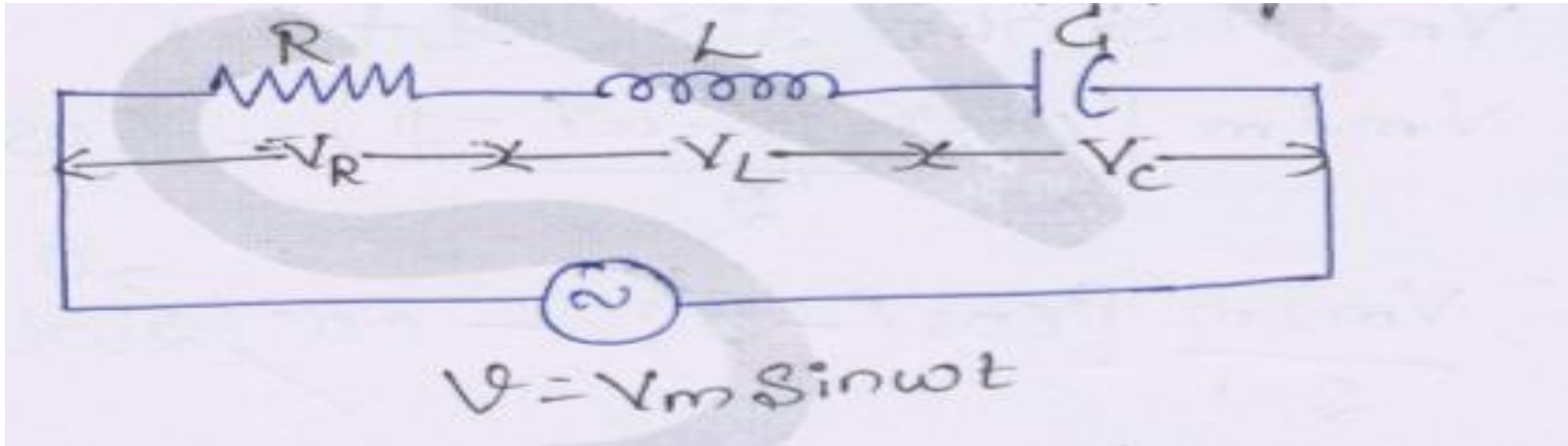
# R-L- C Circuit

Consider an circuit of resistance ' $R$ '  $\Omega$  connected in series with an Inductance of ' $L$ ' Henry and capacitance of ' $C$ ' farads across an A C supply of ' $V$ ' volts.



$$v = V_m \sin \omega t \text{ -----1}$$

$V_R$  = Voltage drop across ' $R$ ',  $V_L$  = Voltage drop across ' $L$ ' and

$V_C$  = Voltage drop across ' $C$ '

$$V_R = IR$$

$$V_L = IX_L \quad \text{where} \quad X_L = 2\pi fL \quad \Omega$$

$$V_C = IX_C \quad \text{where} \quad X_C = 1/2\pi fC \quad \Omega$$


The vector sum

$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$

Phasor diagram



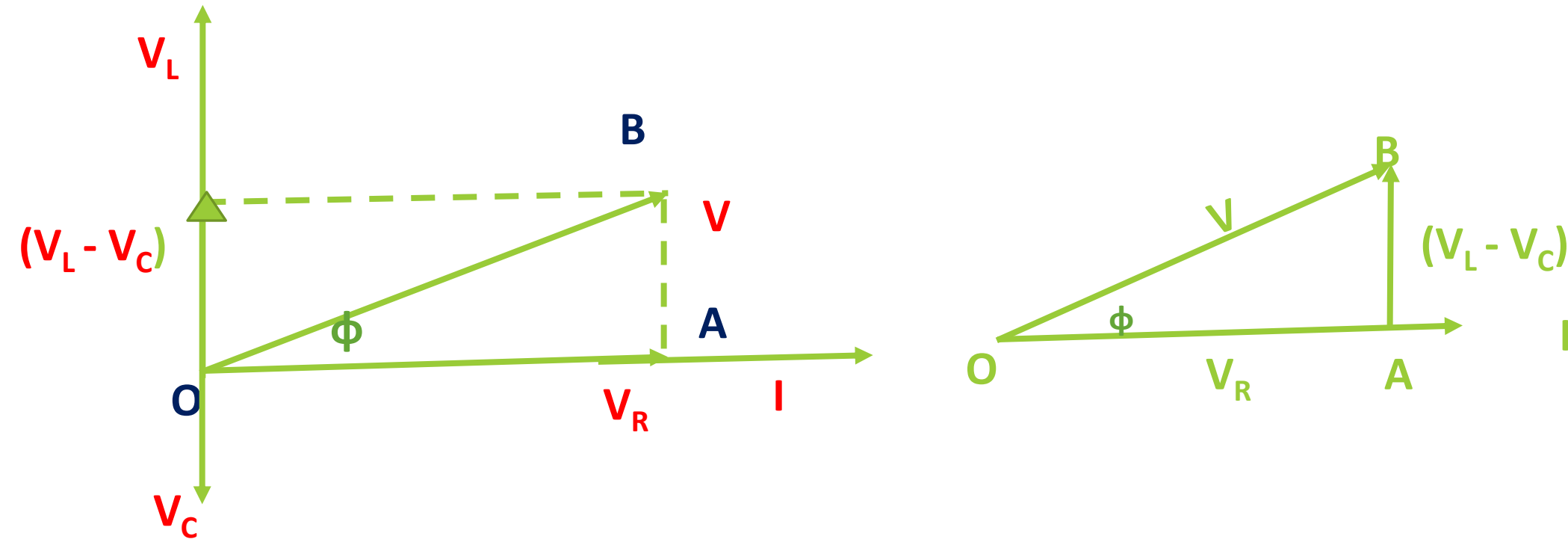Case i) when  $X_L > X_C$  and  $V_L > V_C$




By phasor diagram the current lags the voltage by an angle of ' $\phi$ '.  
Therefore when  $X_L > X_C$  the circuit behaves like inductive circuit.

Consider a triangle OAB

$$\begin{aligned} V &= \sqrt{V_R^2 + (V_L - V_C)^2} = \sqrt{(\dot{I}R)^2 + (IX_L - IX_C)^2} \\ &= I \sqrt{R^2 + (X_L - X_C)^2} \\ \boxed{V = IZ} \quad \text{where} \quad Z &= \sqrt{R^2 + (X_L - X_C)^2} \end{aligned}$$

$$Z = R + jX_L - jX_C \quad \Omega$$

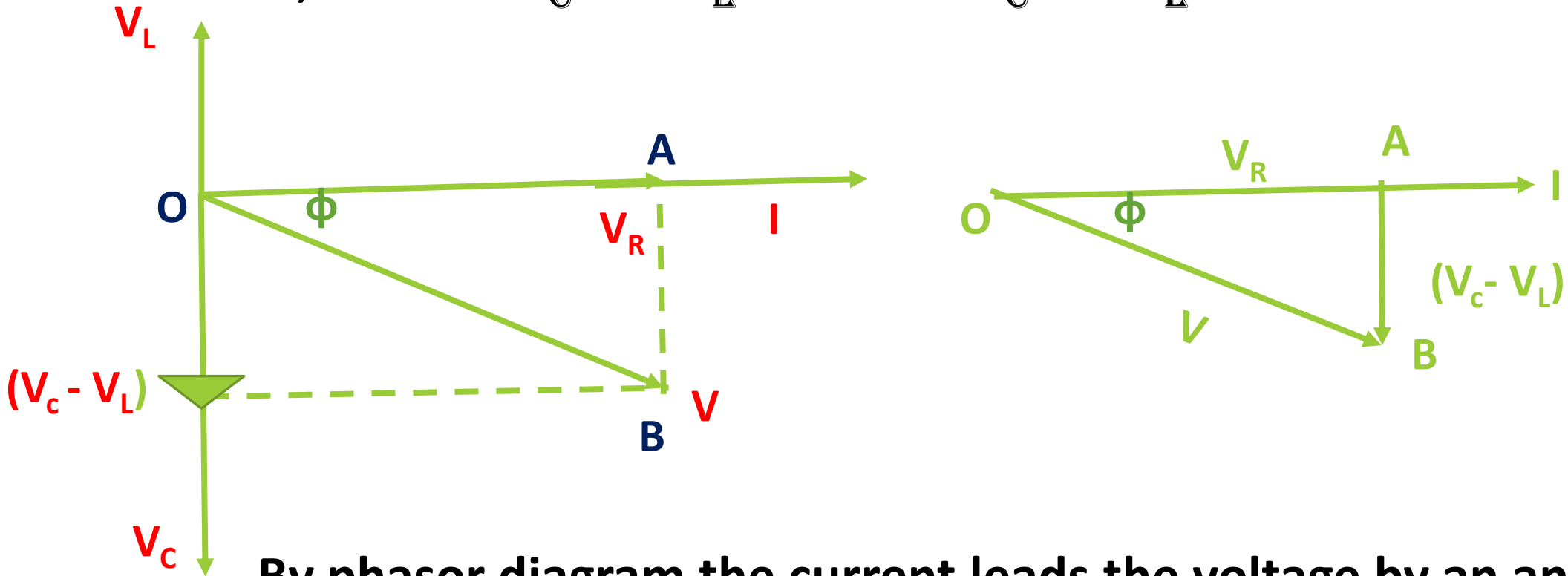Case ii) when  $X_C > X_L$  and  $V_C > V_L$



By phasor diagram the current leads the voltage by an angle of ' $\phi$ ' .

Therefore when  $X_C > X_L$  the circuit behaves like capacitive circuit.

$$V = \sqrt{V_R^2 + (V_C - V_L)^2} = \sqrt{(IR)^2 + (IX_C - IX_L)^2}$$


$$V = I \sqrt{R^2 + (X_C - X_L)^2}$$

$V = IZ$

where  $Z = \sqrt{R^2 + (X_C - X_L)^2}$

$$Z = R + jX_L - jX_C \quad \Omega$$

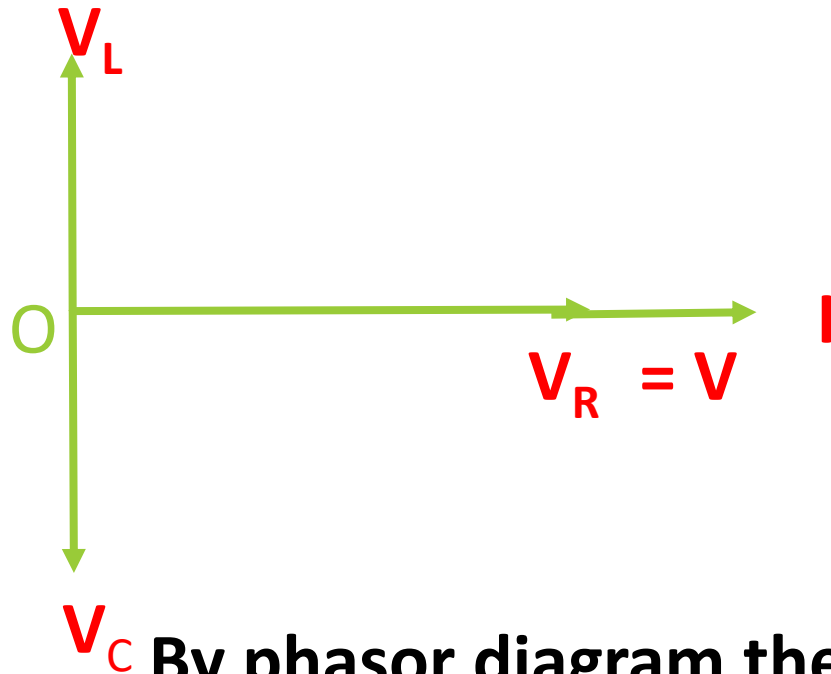Caseiii) when  $X_c = X_L$  and  $V_c = V_L$



$$V = V_R = IR \quad \boxed{Z = R}$$

By phasor diagram the current is in phase with the voltage .  
Therefore when  $X_c = X_L$  the circuit behaves like Resistive circuit.

∴ Case i) when  $X_L > X_C$  it is inductive circuit

Case ii) when  $X_C > X_L$  it is capacitive circuit

Case iii) when  $X_C = X_L$  resistive circuit

# Formulas on R-L-C Circuit

R-L-C Circuit When  $X_L > X_C$       $Z = R + jX_L - jX_C \ \Omega$

$$= \sqrt{R^2 + (X_L - X_C)^2}$$

When  $X_C > X_L$       $Z = R + jX_L - jX_C \ \Omega = \sqrt{R^2 + (X_C - X_L)^2}$

When  $X_L = X_C$       $Z = R$

$$Z = V/I \ \Omega$$

Power factor      $\cos \phi = \frac{R}{Z}$

Active power      $P = V I \cos \phi$  watts

Apparent power      $S = V I$  VA

Reactive power      $Q = V I \sin \phi$  VAR

7. A single phase voltage of  $220+j0$  V, 50Hz applied across the circuit of resistance of  $20\Omega$  and an Inductance of 20mH and capacitance of  $120\mu\text{F}$  are connected in series. Determine the current, power consumed by the circuit, power factor of the circuit and energy stored in an Inductor and draw phasor diagram.

Given:  $V=220+j0 = 220\angle 0$  ,  $f=50\text{Hz}$

$R= 20\Omega$  ,  $L= 20\text{mH} = 20 \times 10^{-3}$  ,  $C= 120\mu\text{F} = 120 \times 10^{-6}$  F and  $I=?$   $P=?$   
 $\text{Pf}=?$  and energy stored in an Inductor  $E=?$

The circuit elements are R, L and C

Therefore  $Z= R +jX_L - jX_C$

$$X_L = 2\pi f L = 2 \times 3.142 \times 50 \times 20 \times 10^{-3} = 6.28\Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.142 \times 50 \times 120 \times 10^{-6}} = 26.52\Omega$$



$$Z = R + jX_L - jX_C = 20 + j6.28 - j26.52$$

$$Z = 20 - j20.24 \, \Omega = 28.45 \angle -45.3$$

$$I = \frac{V}{Z} = \frac{220 \angle 0}{28.45 \angle -45.3} = 7.7 \angle 45.3 \, \text{A}$$

The current is leading the voltage by an angle of  $\phi = 0 - 45.3 = -45.3$

$$\text{Power factor pf} = \cos \phi = \cos(45.3) = 0.703 \quad \text{Leading}$$

$$P = V I \cos \phi = 220 \times 7.7 \times \cos(45.3) = 1191.55 \text{ Watts}$$


$$E = \frac{1}{2} L I^2 = \frac{1}{2} \times 20 \times 10^{-3} \times 7.7^2 = 0.59 \text{ Joules}$$

# Phasor diagram

$$V_R = IR = 7.7 \times 20 = 154V$$

$$V_L = IXL = 7.7 \times 6.28 = 48.36V$$
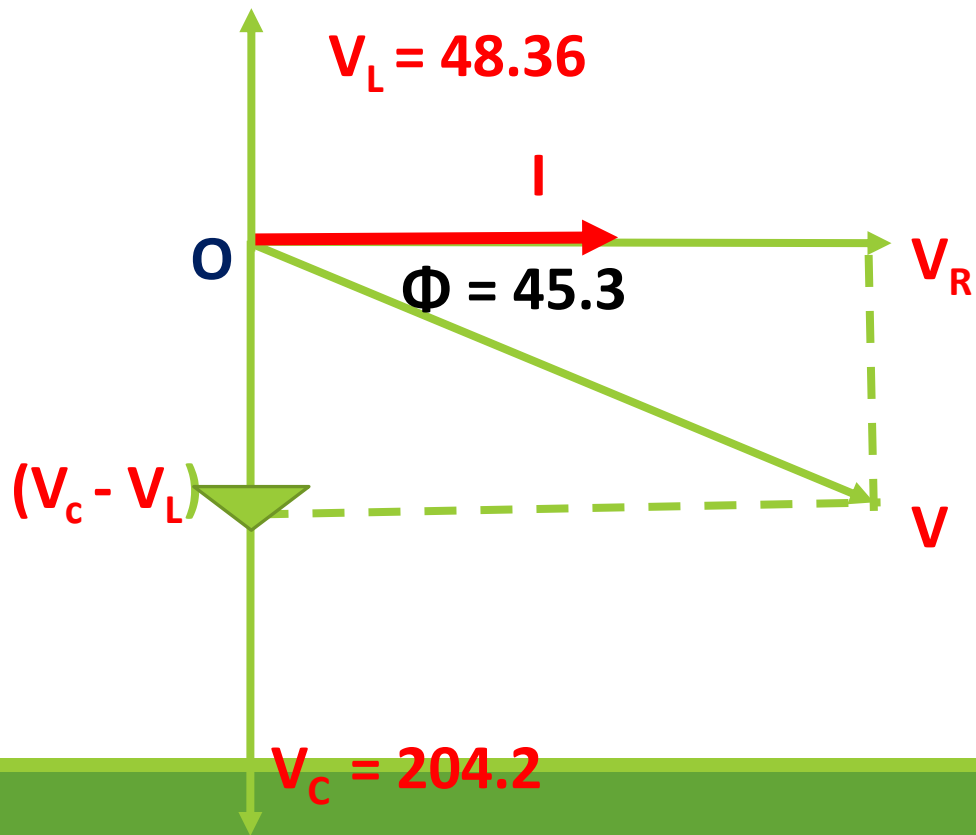
$$V_C = IXC = 7.7 \times 26.52 = 204.2V$$



7) A series RLC circuit is composed of  $100\Omega$  Resistance,  $1\text{ H}$  inductance &  $5\text{ }\mu\text{F}$  capacitance. A voltage  $V(t) = 1414.1 \sin 377t$  Volts is applied to the circuit determine the current impedance & the voltage drop across each element.

Given:-  $V(t) = 1414.1 \sin 377t$  Volts  
 $V_m \sin \omega t$

$R = 100\Omega$        $L = 1\text{ H}$

$C = 5\text{ }\mu\text{F} = 5 \times 10^{-6}\text{ F}$

$V_m = 1414.1\text{ V}$

$\omega = 2\pi f = 377$

$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{1414.1}{\sqrt{2}}$

$377 = 2\pi \times 3.142 \times f$

$f = \frac{377}{2\pi \times 3.142}$

$f = 60\text{ Hz}$

$V_{rms} = V = 1000\text{ V}$

$$Z = R + jX_L - jX_C$$

$$Z = 100 + j376.8 - j530.78$$

$$Z = 100 - j246$$

$$Z = 183.6 \angle -56.99^\circ \Omega$$

$$X_L = 2\pi fL$$

$$= 2 \times 3.142 \times 60 \times 1$$

$$X_L = 376.8 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.142 \times 60 \times 5 \times 10^{-6}}$$

$$X_C = 530.78 \Omega$$

$$I = \frac{V}{Z} = \frac{1000 \angle 0^\circ}{183.6 \angle -56.99^\circ} = 5.44 \angle 56.99^\circ$$

$$\rightarrow \phi = 56.99^\circ$$

$$V_R = IR = 5.44 \times 100 = 544 \text{ V}$$

$$V_L = IX_L = 5.44 \times 376.8 = 2034.79 \text{ V}$$

$$V_C = IX_C = 5.44 \times 530.78 = 2866.21 \text{ V}$$

# Module -2b : Three Phase AC Circuit

---


# Advantages of 3- phase over single phase

1. The output of the three phase machine is always greater than single phase machine of the same size.
2. The 3- $\phi$  system gives a steady output.
3. The three phase motor is self started where as single phase motors are not self started.
4. The single phase can be obtained by 3-phase but 3-phase cannot be obtained by 1- $\phi$ .
5. For transmission and distribution , three phase system requires less copper or conducting material compare to 1-phase .
6. The power factor of the single phase motor is poor than 3-phase motors.



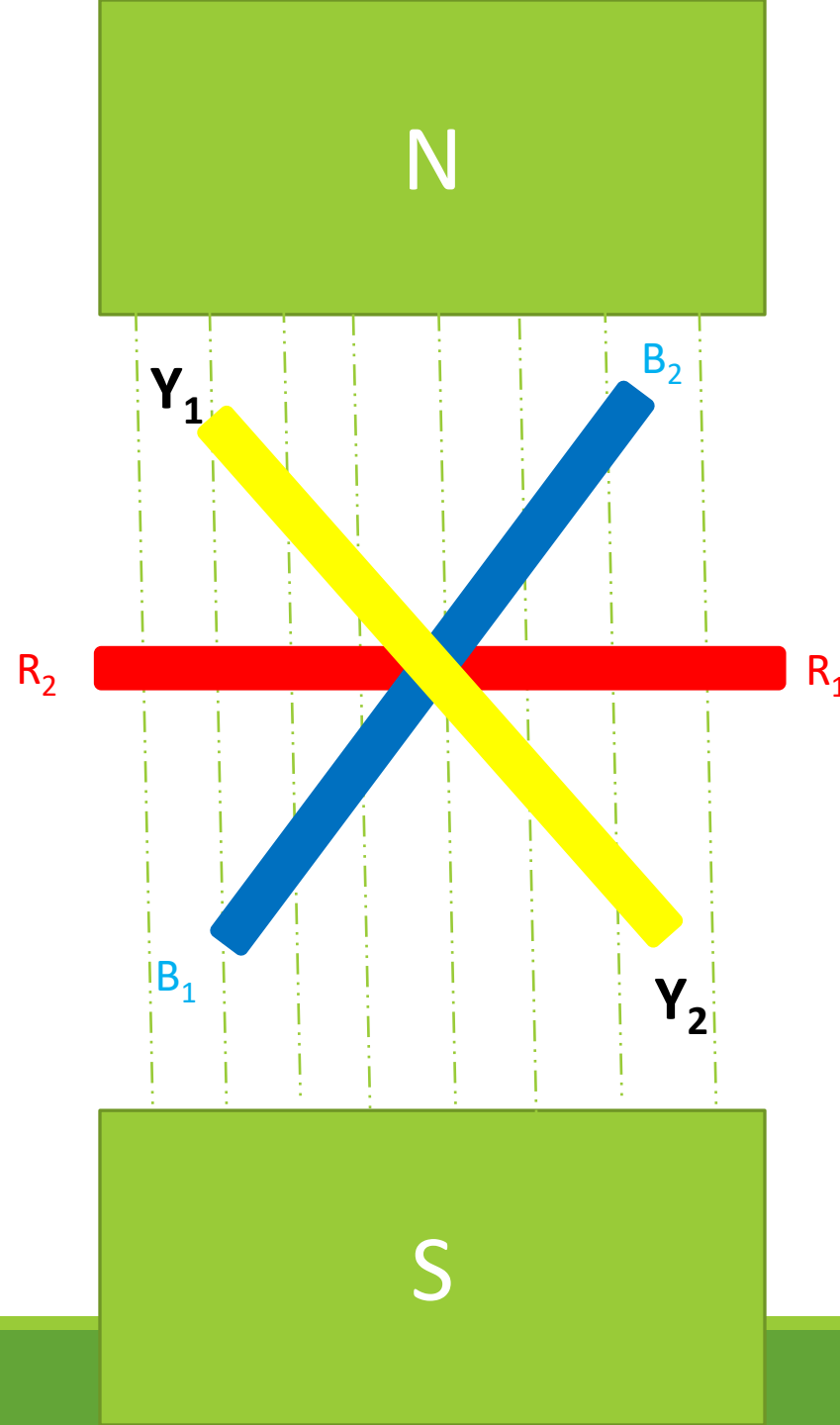
## Generation of 3-phase voltage system


- Consider an armature winding are divided into 3 groups of an alternator they are displaced by an angle of  $120^\circ$  from each other, three alternating voltages are developed as shown in fig.
- The coils are named as R1-R2, Y1-Y2 and B1-B2





- Let  $e_R$ ,  $e_Y$  and  $e_B$  are voltages induced in the coil R1-R2, Y1-Y2 and B1-B2 respectively
- All the voltages are of same magnitude and frequency but they are displaced by  $120^\circ$  apart from each other.
- Let us assume  $e_R$  are the reference the equations of the induced emf's are
- $e_R = E_m \sin \omega t$**
- $e_Y = E_m \sin(\omega t - 120)$
- $e_B = E_m \sin(\omega t - 240) = E_m (\sin \omega t + 120)$**

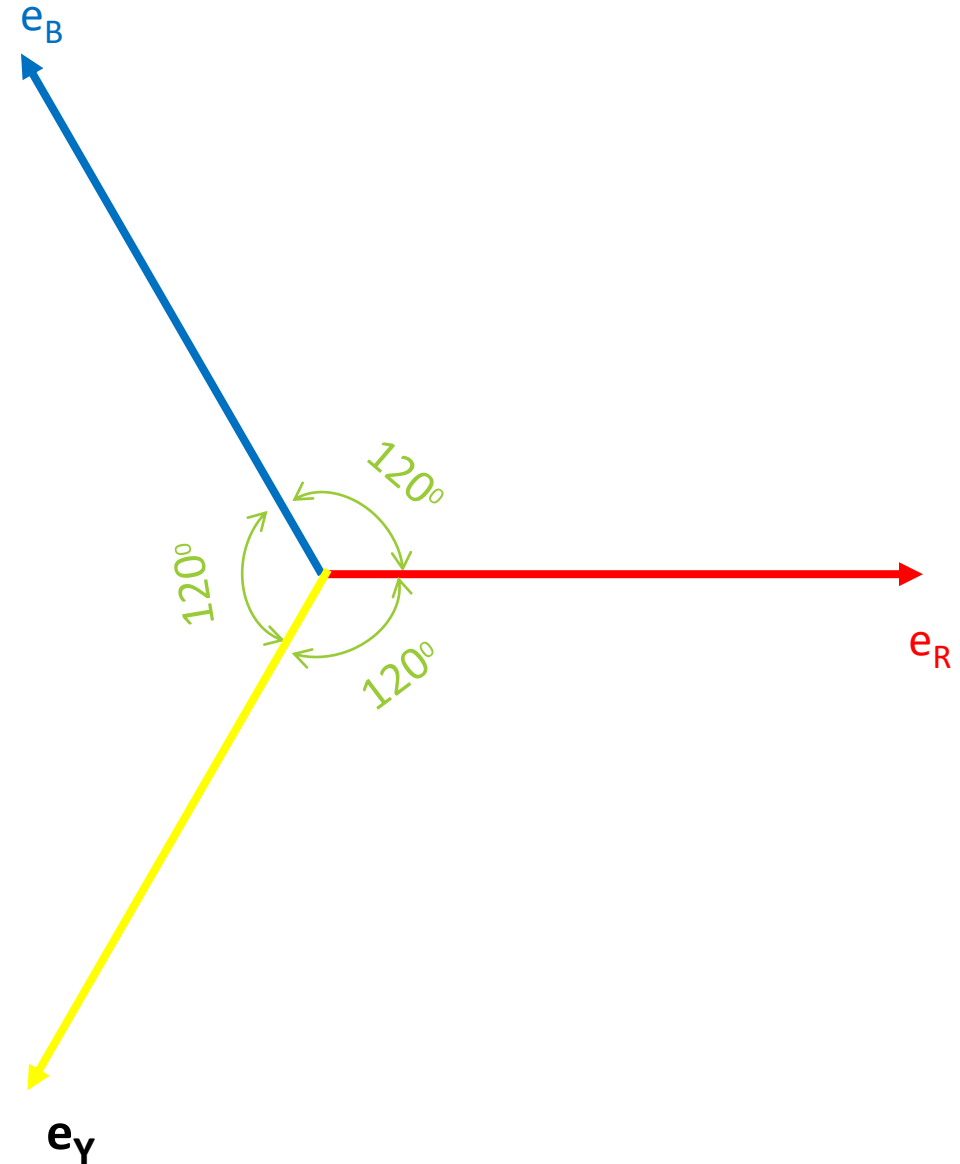


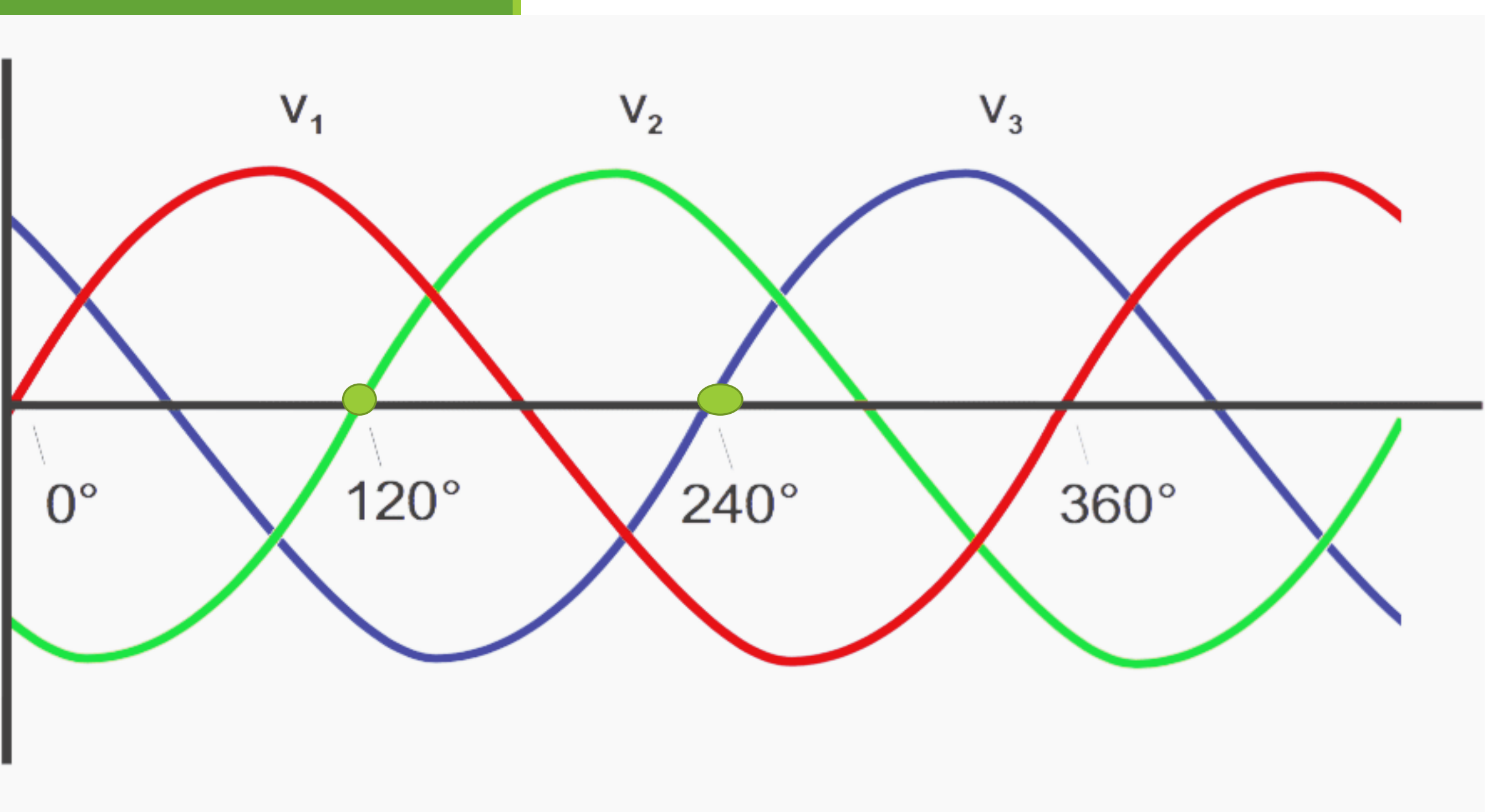

# Three phase Load Connection
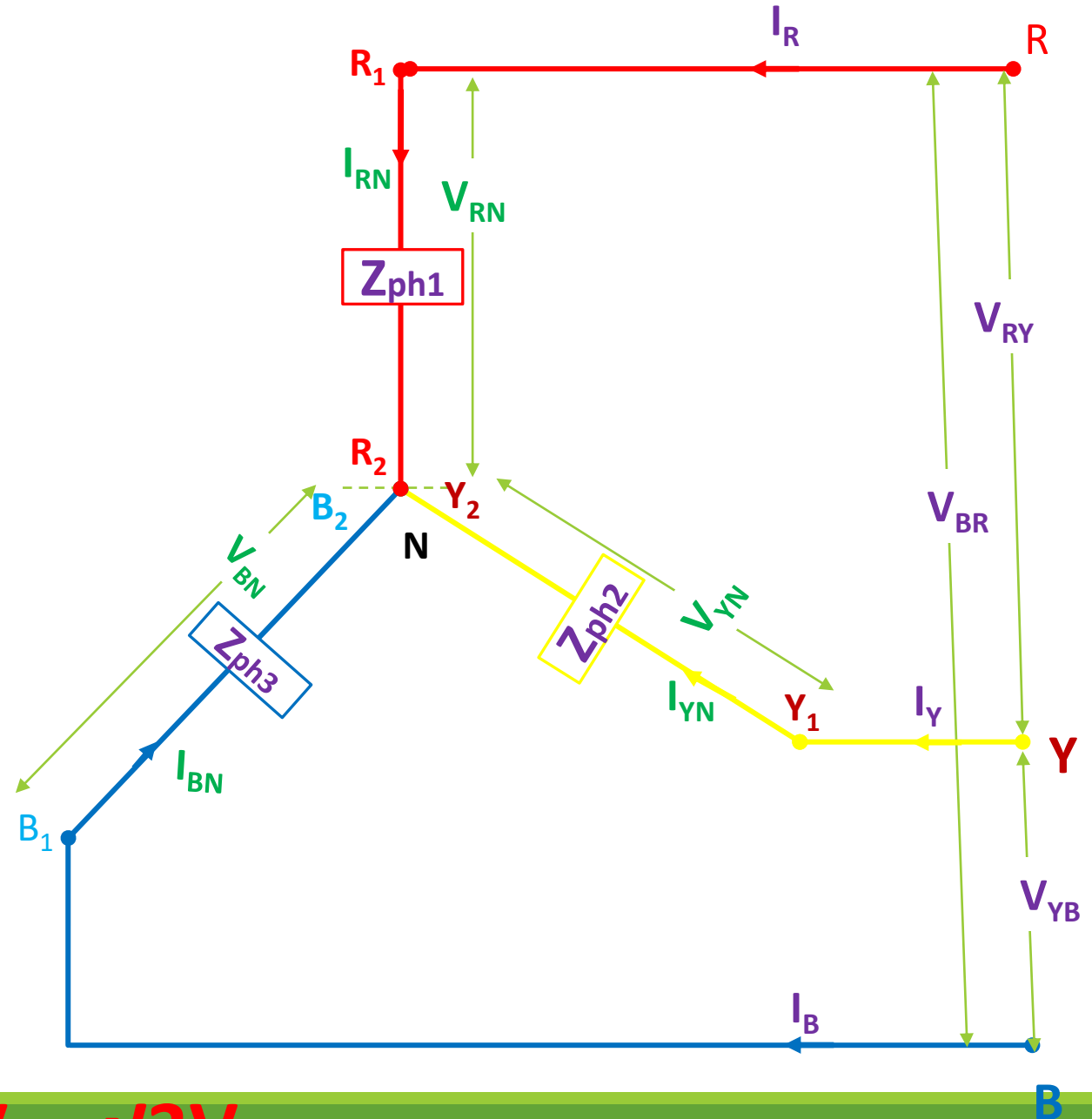
## STAR CONNECTION


- The star connection is formed by connecting terminating ends of all the three windings together at a common point called **Neutral (N)**.
- I.e R2, Y2 and B2 together.**
- The remaining ends brought together for supply connections **I.e to R-Y-B.**
- The connection is as shown in the fig.
- $V_{RY}$ ,  $V_{YB}$  and  $V_{BR}$  are line voltages
- $I_R$ ,  $I_Y$  and  $I_B$  are line currents.
- $V_{RN}$ ,  $V_{YN}$  and  $V_{BN}$  are Phase voltages
- $I_{RN}$ ,  $I_{YN}$  and  $I_{BN}$  are phase currents



In star connection  $I_L = I_{ph}$  and  $V_L = \sqrt{3}V_{ph}$
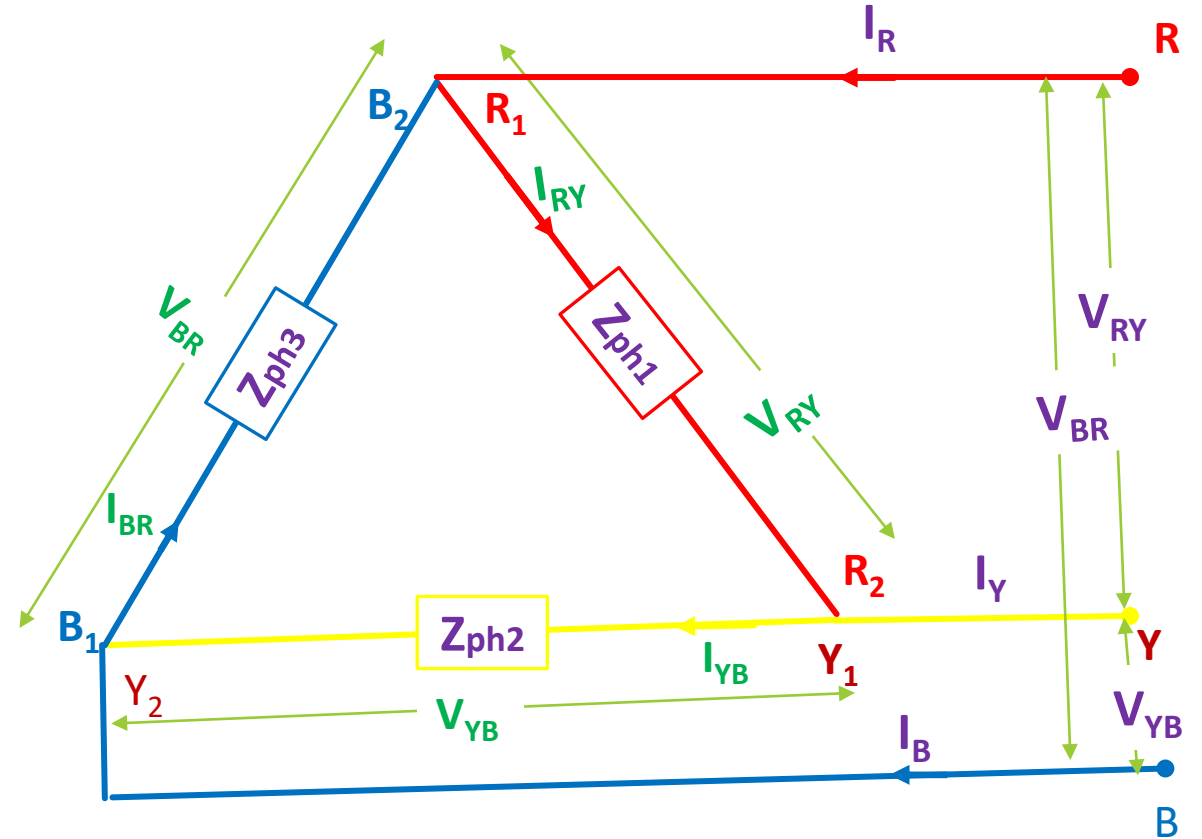
# DELTA CONNECTION

- The delta connection is formed by connecting the terminating end of one winding to starting end of the another winding to form a closed loop.
- The supply connection is taken out from each junction.
- The connection is as shown in the fig.
- $V_{RY}$ ,  $V_{YB}$  and  $V_{BR}$  are line voltages
- $I_R$ ,  $I_Y$  and  $I_B$  are line currents.
- $V_{RY}$ ,  $V_{YB}$  and  $V_{BR}$  are Phase voltages
- $I_{RY}$ ,  $I_{YB}$  and  $I_{BR}$  are phase currents



In delta connection  $I_L = \sqrt{3}I_{ph}$  and  $V_L = V_{ph}$

# List of formulas

1. In star connection  $I_L = I_{ph}$  and  $V_L = \frac{1}{\sqrt{3}} V_{ph}$
2. In delta connection  $I_L = \sqrt{3} I_{ph}$  and  $V_L = V_{ph}$
3.  $P = \sqrt{3} V_L I_L \cos \Phi$  Watt or  $P = 3 V_{ph} I_{ph} \cos \Phi$
4.  $Q = \sqrt{3} V_L I_L \sin \Phi$  VAR
5.  $S = \sqrt{3} V_L I_L$  VA

# Formulas

For R-L circuit:  $z = R + jX_L$  where  $X_L = 2\pi fL \Omega$

For R-C circuit:  $z = R - jX_C$  where  $X_C = 1/2\pi fC \Omega$

For R- L -C circuit:  $z = R + jX_L - jX_C$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}}$$

[Note: Unless the voltage is mentioned as phase voltage take it as a line voltage]

Star connection is also denoted as -  $Y$

Delta connection is also denoted as -  $\Delta$

1. A balanced star connected load of  $(8+j6)\Omega$  is connected to a 3- $\phi$  230V supply. Find the line current, phase current, power factor, active power, reactive volt ampere, total volt ampere.

Given :  $Z_{ph} = 8+j6 = 10\angle 36.86^\circ \Omega$  (star connected)

$$V_L = 230\angle 0^\circ$$

$$I_L = ? \quad I_{ph} = ? \quad pf = ? \quad P = ? \quad Q = ? \quad S = ?$$

In star connection :  $I_L = I_{ph}$  and  $V_L = \sqrt{3}V_{ph}$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{230\angle 0^\circ}{\sqrt{3}} = 132.79 \angle 0^\circ \text{ V}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{132.79\angle 0^\circ}{10\angle 36.86^\circ} = 13.27 \angle -36.86^\circ \text{ A}$$

$$I_L = I_{ph} = 13.27 \angle -36.86^\circ \text{ A}$$

$$\Phi = 0 - (-36.86) = 36.86$$

$$\cos \phi = \cos(36.86) = 0.8 \text{ lagging}$$

$$P = \sqrt{3} V_L I_L \cos \Phi = \sqrt{3} * 230 * 13.27 * 0.8 = 4.2 \text{ KW}$$

$$Q = \sqrt{3} V_L I_L \sin \Phi = \sqrt{3} * 230 * 13.27 * \sin(36.86) = 3.1 \text{ KVAR}$$

$$S = \sqrt{3} V_L I_L = \sqrt{3} * 230 * 13.27 = 5.2 \text{ KVA}$$



2. A balanced Delta connected load of  $(8+j6)\Omega$  is connected to a 3- $\phi$  230V supply. Find the line current, phase current, power factor, active power, reactive volt ampere, total volt ampere.

Given :  $Z_{ph} = 8+j6 = 10\angle 36.86^\circ \Omega$  (Delta connected)

$$V_L = 230\angle 0^\circ$$

$$I_L = ? \quad I_{ph} = ? \quad \text{pf} = ? \quad P = ? \quad Q = ? \quad S = ?$$

In Delta connection :  $V_L = V_{ph}$  and  $I_L = \sqrt{3}I_{ph}$

$$V_L = V_{ph} = 230\angle 0^\circ \text{V}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230\angle 0^\circ}{10\angle 36.86^\circ} = 23\angle -36.86^\circ \text{A}$$

$$I_L = \sqrt{3} I_{ph} = \sqrt{3} * 23 \angle -36.86 = 39.83 \angle -36.86 \text{ A}$$

$$\Phi = 0 - (-36.86) = 36.86$$

$$\cos \phi = \cos(36.86) = 0.8 \text{ lagging}$$

$$P = \sqrt{3} V_L I_L \cos \Phi = \sqrt{3} * 230 * 39.83 * 0.8 = 12.6 \text{ KW}$$

$$Q = \sqrt{3} V_L I_L \sin \Phi = \sqrt{3} * 230 * 39.83 * \sin(36.86) = 9.3 \text{ KVAR}$$

$$S = \sqrt{3} V_L I_L = \sqrt{3} * 230 * 39.83 = 15.86 \text{ KVA}$$

3. A resistance of 100 ohms is connected in series with an inductance of 1mH in each phase of a 400V star connected 50Hz three phase supply. Calculate i) impedance per phase (ii) Total current (iii) power factor (iv) active power (v) reactive power (vi) apparent power.

**Given:**  $R = 100$ ,  $L = 1\text{mH} = 1 \times 10^{-3}\text{H}$  ,

$V_L = 400 \angle 0^\circ \text{ V}$ ,  $f = 50\text{Hz}$

$Z_{ph} = ?$  ,  $I_L = ?$  ,  $\cos \Phi = ?$  ,  $P = ?$  ,  $Q = ?$  ,  $S = ?$

The phase consists of R in series with L  $Z_{ph} = R + j X_L$

$$X_L = 2\pi fL = 2 * 3.142 * 50 * 1 \times 10^{-3} = 0.314\Omega$$

$$Z_{ph} = R + j X_L = 100 + j0.314 = 100 \angle 0.179^\circ \Omega$$

In star connection :  $I_L = I_{ph}$  and  $V_L = \sqrt{3}V_{ph}$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400 \angle 0^\circ}{\sqrt{3}} = 230.94 \angle 0^\circ \text{ V}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.94 \angle 0}{100 \angle 0.179} = 2.3 \angle -0.179 \text{ A}$$

$$I_L = I_{ph} = 2.3 \angle -0.179 \text{ A}$$

$$\Phi = 0 - (-0.179) = 0.179$$

$$\cos \Phi = \cos (0.179) = 0.99 \text{ lagging}$$

$$P = \sqrt{3} V_L I_L \cos \Phi = \sqrt{3} * 400 * 2.3 * 0.99 = 1577.55 = 1.5 \text{ KW}$$

$$Q = \sqrt{3} V_L I_L \sin \Phi = \sqrt{3} * 400 * 2.3 * \sin(0.179) = 4.978 \text{ VAR},$$

$$S = \sqrt{3} V_L I_L = \sqrt{3} * 400 * 2.3 = 1593.48 \text{ VA}$$

4. A resistance of 50 ohms is connected in series with a capacitance of  $150\mu\text{F}$  in each phase of a 450V delta connected 50Hz three phase supply. Calculate capacitive reactance (ii) impedance per phase (iii) line current and phase current (iv) power factor (v) active power (vi) reactive power (vii) apparent power.

**Given :**  $R = 50 \Omega$   $C = 150 \mu\text{F} = 150 \times 10^{-6} \text{ F}$   $V_L = 450 \angle 0$

$$X_c = 1 / 2\pi fC = \frac{1}{2 * \pi * 50 * 150 * 10^{-6}} = 21.22 \Omega$$

$$Z_{ph} = R - j X_c = 50 - j21.22 = 54.31 \angle -22.99$$

In Delta connection :  $V_L = V_{ph}$  and  $I_L = \sqrt{3} I_{ph}$

$$V_L = V_{ph} = 450 \angle 0$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{450 \angle 0}{54.31 \angle -22.99} = 8.28 \angle 22.99 \text{ A}$$

$$I_L = \sqrt{3} I_{ph} = \sqrt{3} * 8.28 \angle 22.99 = 14.34 \angle 22.99 \text{ A}$$

$$\Phi = 0 - 22.99 = -22.99$$

$$\cos \Phi = \cos (-22.99) = 0.92 \text{ leading}$$

$$P = \sqrt{3} V_L I_L \cos \Phi = \sqrt{3} * 450 * 14.34 * 0.92 = 10282.76 \text{ W} = 10.28 \text{ KW}$$

$$Q = \sqrt{3} V_L I_L \sin \Phi = \sqrt{3} * 450 * 14.34 * \sin(22.99) = 4365.37 \text{ VAR}$$

$$S = \sqrt{3} V_L I_L = \sqrt{3} * 450 * 14.34 = 11176.92 \text{ VA}$$

5. Arms of a 3- $\phi$  load consists of an inductor of 0.15H and a resistance of 25 $\Omega$  and capacitance of 120 $\mu$ F are connected series the supply voltage is 415V, 50Hz ,the load is connected in delta. Calculate the line current ,phase current, power and reactive power.

**Given :** R =25  $\Omega$ , L= 0.15 H ,C = 120  $\mu$  F = 120  $\times 10^{-6}$  F ,  $V_L = 415\angle 0$  ,  
f=50Hz

$I_L = ?$      $I_{ph} = ?$     P= ?    Q=?

The phase consists of R in series with L and C     $Z_{ph} = R + j X_L - jX_C$

$$X_L = 2\pi fL = 2 * 3.142 * 50 * 0.15 = 47.13\Omega$$

$$X_C = 1 / 2\pi fC = \frac{1}{2 * \pi * 50 * 120 * 10^{-6}} = 26.56 \Omega$$

$$Z_{ph} = R + j X_L - jX_C = 25 + j47.13 - j26.56$$

$$Z_{ph} = 25 + j20.57 = 32.37\angle 39.44 \Omega$$

In Delta connection :  $V_L = V_{ph}$  and  $I_L = \sqrt{3}I_{ph}$

$$V_L = V_{ph} = 415 \angle 0^\circ \text{ V}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{415 \angle 0^\circ}{32.37 \angle 39.44^\circ \Omega} = 12.81 \angle -39.44^\circ \text{ A}$$

$$I_L = \sqrt{3}I_{ph} = \sqrt{3} * 12.81 \angle -39.44^\circ = 22.18 \angle -39.44^\circ \text{ A}$$

$$\Phi = (0 - (-39.44)) = 39.44^\circ$$

$$\cos \Phi = \cos (39.44^\circ) = 0.77 \text{ lagging}$$

$$P = \sqrt{3} V_L I_L \cos \Phi = \sqrt{3} * 415 * 22.18 * 0.77 = 12312.6 \text{ W} = 12.312 \text{ KW}$$

$$Q = \sqrt{3} V_L I_L \sin \Phi = \sqrt{3} * 415 * 22.18 * \sin(39.44^\circ) = 10128.12 \text{ VAR}$$